

LAB NOTE

Subject: Digital Design Principles

Topic: Parking Indicator

Student: Minh Quan Tran

May 24th, 2024

Table of Contents

- 1. Objectives 4**
- 2. Design 6**
 - 2.1 Requirement 6
 - 2.2 Solution 6
- 3. VHDL and Verilog 6**
 - 3.1 VHDL code 6
 - 3.2 Verilog code 7
- 4. Pin Planner..... 8**
 - 4.1 Input and Output..... 8
- 5. Result 10**

TABLE OF FIGURES

Figure 4-1: SCEMA5F31C6N board	8
Figure 4-2: SW0 and SW1 Pin No	9
Figure 4-3: LEDR0's Pin No	9
Figure 4-4: HEX's Pin No	9
Figure 5-1: When all 6 levels are available.	10
Figure 5-2: When 1 level is full.....	10
Figure 5-3: When all levels are full.....	11

1. Objectives

1. Objectives

- Design a parking indicator using Quartus software.
- Write a VHDL and Verilog code from the design.
- Push the code and run to the SCEMA5F31C6N board.

2. Design

2. Design

2.1 Requirement

Procedure:

Consider the following parking control system:

A parking lot is constructed of 6 levels; each level has 16 parking spaces. At the entrance there is red light indicator. When all the parking spaces (in the 6 levels) are occupied, the red-light indicator is ON and the green Light indicator is OFF, when there is an available parking space at any level the red light indicator is OFF and the green light indicator is ON.

Hint: This is a two stages design, you need to design only the second stage.

1. Create a new project targeting your FPGA (follow naming criteria)
2. Create a top level VHDL file containing 6 switch inputs, and 1 led Red output.
3. For the Library section you will need:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
4. For the Entity section, use the following information:
SW [0:5] – Input Switches.
LEDR [2] – Red Output indicator.
LEDG [3] – Green Output indicator.
5. In the architecture section, in a process block sensitive to the switch inputs, describe combinational logic for the system.
6. From the Processing menu, run Start->Start Analysis & Synthesis
7. Assign the LED and SW pins from Assignments -> Pin Planner
8. Place and route the design using Processing ->Start Compilation.
9. Download your design to your FPGA.
10. When your design is working on the FPGA, demonstrate it to the instructor.

2.2 Solution

From the Hint, it indicates that there are 2 stages to design,

- First would be the design for each level indicating if there are free slots left.
- Second, will be the design for overall system in which if all levels are occupied then the red LED will light up and the green LED will turn off.

Because it is only required to design for the second stage, so the number of input and output for this system will be:

- Input: 6 levels each will be described as SW0 to SW6 by the board.
- Output: 2 LED, LEDR0 is for green LED and LEDR1 is for red LED.

It states that: “When **all** the parking spaces (in the 6 levels) are occupied, the red-light indicator is ON and the green Light indicator is OFF”, so AND gate with 6 inputs will be best suited for this job.

Also “When there is an available parking space at any level the red-light indicator is OFF, and the green light indicator is ON.” So, the output for red LED is the opposite of green LED.

3. VHDL and Verilog

3.1 VHDL code

```
library ieee;
use ieee.std_logic_1164.all;

-- Declaring input and output
entity MTran_Lab3_VHDL_ParkIndicator is
    port
    (
        SW : in  std_logic_vector (5 downto 0);
        LED: out std_logic_vector (0 to 1);
        HEX: out std_logic_vector (6 downto 0)
    );
end MTran_Lab3_VHDL_ParkIndicator;

-- Describing the relationship between output and input
architecture behavioral of MTran_Lab3_VHDL_ParkIndicator is

    shared variable free_slot: integer := 0;
begin

    -- Counting free slot in parking
    process (SW)
    begin

        -- Resetting free_slot
        free_slot := 0;

        -- Counting free slot in parking
        for i in SW'range loop
            if SW(i) = '0' then
                free_slot := free_slot + 1;
            end if;
        end loop;

        -- Displayed number of free slot to 7 segment LED
        case free_slot is
            when 0 => HEX <= "1000000";
            when 1 => HEX <= "1111001";
            when 2 => HEX <= "0100100";
            when 3 => HEX <= "0110000";
            when 4 => HEX <= "0011001";
            when 5 => HEX <= "0010010";
            when 6 => HEX <= "0000010";
            when others => HEX <= "1111111";
        end case;

        -- Displaying LED
        case (SW) is
            when "111111" => LED <= "10";
            when others   => LED <= "01";
        end case;

    end process;

end behavioral;
```

3. VHDL and Verilog

3.2 Verilog code

```
module MTran_Lab3_Verilog_ParkIndicator(  
    input wire [5:0] SW,  
    output reg [1:0] LED,  
    output reg [6:0] HEX  
);  
    // declaring a vector to store 7 Segment LED code  
    reg [6:0] LED_code[15:0];  
    integer i = 0;  
    integer free_slot = 0;  
  
    // initializing declaration  
    initial begin  
        LED_code[0] = 7'h40; //0 // can't use 0x40 have to be 7'h or 7'b,...  
        LED_code[1] = 7'h79; //1  
        LED_code[2] = 7'h24; //2  
        LED_code[3] = 7'h30; //3  
        LED_code[4] = 7'h19; //4  
        LED_code[5] = 7'h12; //5  
        LED_code[6] = 7'h02; //6  
        LED_code[7] = 7'h78; //7  
        LED_code[8] = 7'h00; //8  
        LED_code[9] = 7'h10; //9  
        LED_code[10] = 7'h08; //A  
        LED_code[11] = 7'h03; //b  
        LED_code[12] = 7'h46; //C  
        LED_code[13] = 7'h21; //d  
        LED_code[14] = 7'h06; //E  
        LED_code[15] = 7'h0E; //F  
    end  
  
    // always block (execute again when there are change in variable)  
    always @(*)  
    begin  
  
        //Resetting variable free_Slot  
        free_slot = 0;  
  
        // Check how many free slot remain  
        for (i = 0; i < 6; i = i + 1)  
        begin  
            if (SW[i] == 0)  
            begin  
                free_slot = free_slot + 1;  
            end  
        end  
  
        //Display remaining free slot on 7 segment led  
        HEX = LED_code[free_slot];  
  
        //Displaying LED  
        case (SW)  
            6'b111111: LED = 2'b10;  
            default: LED = 2'b01;  
        endcase  
    end  
endmodule
```

4. Pin Planner

4.1 Input and Output

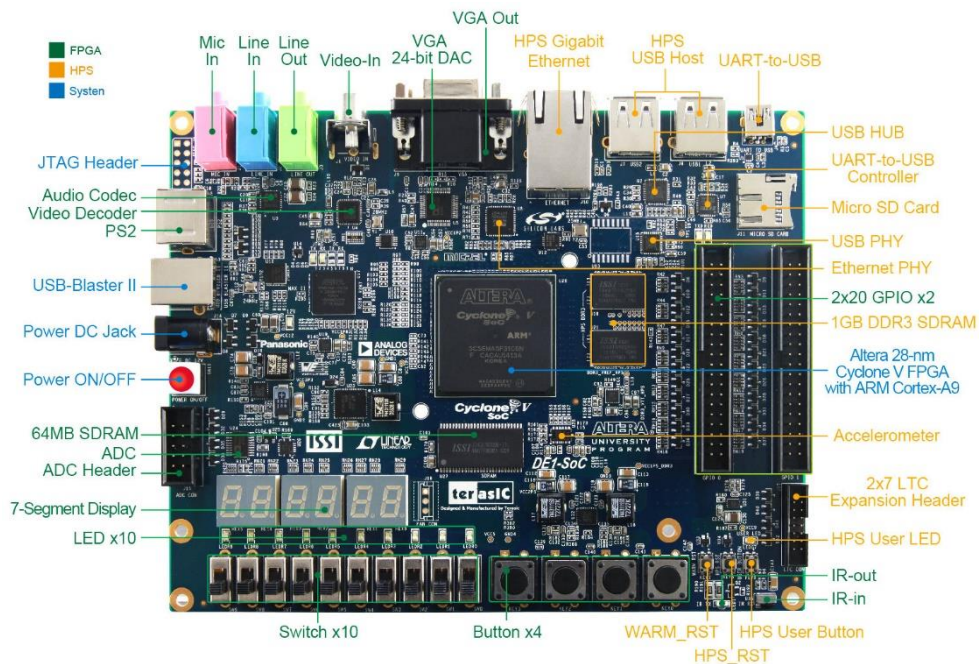


Figure 4-1: SCEMA5F31C6N board

Assigning:

SW[0]: SW0
SW[1]: SW1
SW[2]: SW2
SW[3]: SW3
SW[4]: SW4
SW[5]: SW5

LED[0]: LEDR0
LED[1]: LEDR1

HEX[0]: HEX0[0]
HEX[1]: HEX0[1]
HEX[2]: HEX0[2]
HEX[3]: HEX0[3]
HEX[4]: HEX0[4]
HEX[5]: HEX0[5]
HEX[6]: HEX0[6]

From the DE1_SoC_User_Manual,

4. Pin Planner

<i>Signal Name</i>	<i>FPGA Pin No.</i>	<i>Description</i>	<i>I/O Standard</i>
SW[0]	PIN_AB12	Slide Switch[0]	3.3V
SW[1]	PIN_AC12	Slide Switch[1]	3.3V
SW[2]	PIN_AF9	Slide Switch[2]	3.3V
SW[3]	PIN_AF10	Slide Switch[3]	3.3V
SW[4]	PIN_AD11	Slide Switch[4]	3.3V
SW[5]	PIN_AD12	Slide Switch[5]	3.3V

Figure 4-2: SW0 and SW1 Pin No

<i>Signal Name</i>	<i>FPGA Pin No.</i>	<i>Description</i>	<i>I/O Standard</i>
LEDR[0]	PIN_V16	LED [0]	3.3V
LEDR[1]	PIN_W16	LED [1]	3.3V

Figure 4-3: LEDR0's Pin No

<i>Signal Name</i>	<i>FPGA Pin No.</i>	<i>Description</i>	<i>I/O Standard</i>
HEX0[0]	PIN_AE26	Seven Segment Digit 0[0]	3.3V
HEX0[1]	PIN_AE27	Seven Segment Digit 0[1]	3.3V
HEX0[2]	PIN_AE28	Seven Segment Digit 0[2]	3.3V
HEX0[3]	PIN_AG27	Seven Segment Digit 0[3]	3.3V
HEX0[4]	PIN_AF28	Seven Segment Digit 0[4]	3.3V
HEX0[5]	PIN_AG28	Seven Segment Digit 0[5]	3.3V
HEX0[6]	PIN_AH28	Seven Segment Digit 0[6]	3.3V

Figure 4-4: HEX's Pin No

5. Result

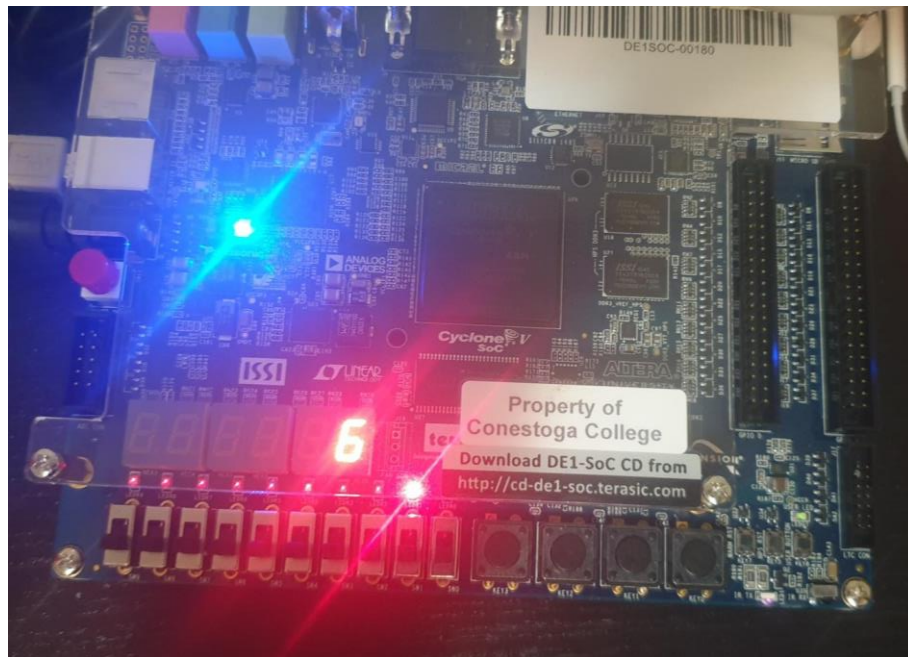


Figure 5-1: When all 6 levels are available.

All SW are off, mean that all levels are available for parking, 7 segments LED displays '6' mean that there are 6 levels available for parking.

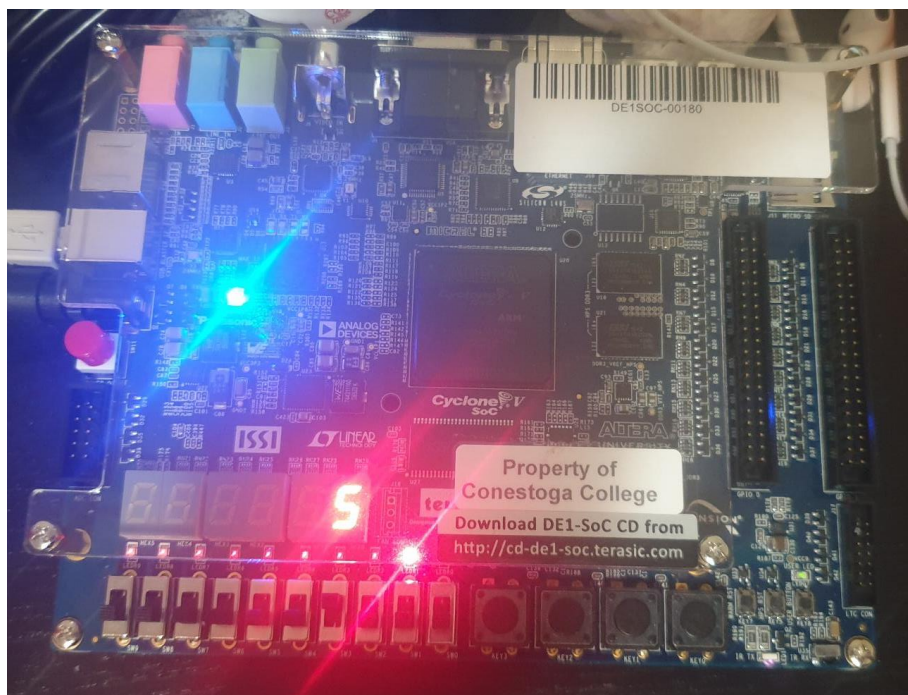


Figure 5-2: When 1 level is full

When turn on SW3, LEDR1 remained ON indicating there still slot available in this parking slot and the 7 segments LED display '5' which mean there are '5' levels available.

5. Result

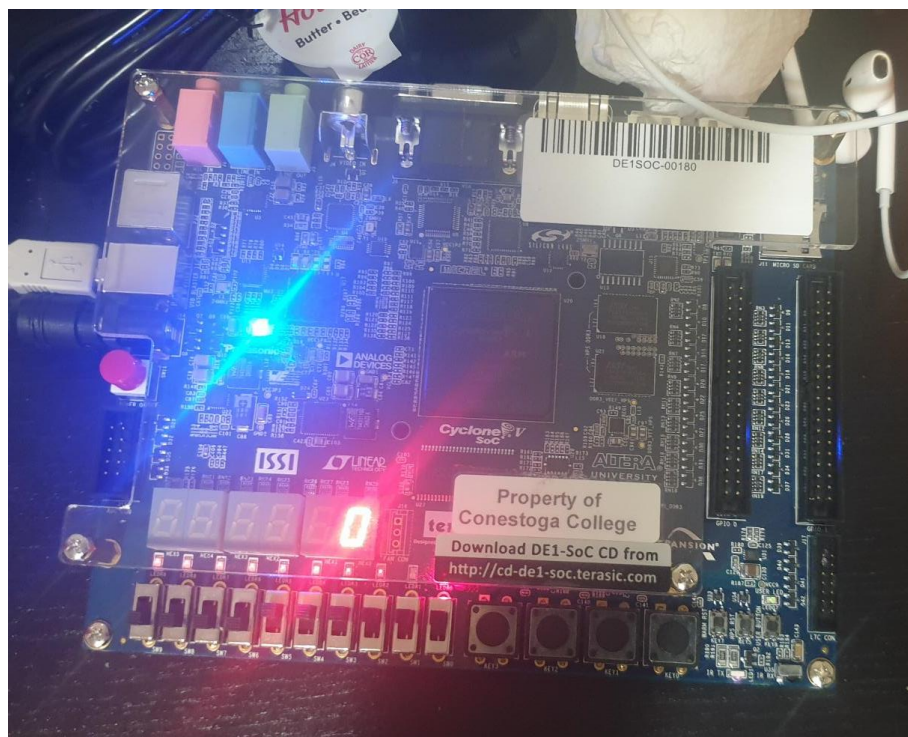


Figure 5-3: When all levels are full

When all levels are full LEDR1 turns off and LEDR0 turn on indicating it full and the 7 segments LED display '0' which mean no more slots are available.

REFERENCES