

LAB NOTE

Subject: Electronic Design Principles

Topic: Scale Adder

Student: Minh Quan Tran

June 7th, 2024

Table of Contents

- 1. Objectives 4
- 2. Theory and Calculation 5
 - 2.1 Theory 5
 - 2.2 Design and Calculation 5
- 3. Design and Result 6
 - 3.1 Multisim’s design. 6
 - 3.2 Breadboard’s design 6
 - 3.3 Result..... 7
 - 3.3.1 DC power 7
 - 3.3.2 AC power 8
- 4. CONCLUSION..... 9

TABLE OF FIGURES

Figure 2-1: Scale Adder's design.....	5
Figure 2-2: LM348N's datasheet	6
Figure 3-1: Multisim's design.....	6
Figure 3-2: Breadboard's design	6

~~~~~

## TABLE'S OF TABLE

|                                          |   |
|------------------------------------------|---|
| Table 3-1: DC power for Scale Adder..... | 7 |
| Table 3-4: AC power for Scale Adder..... | 8 |

## 1. Objectives

---

### 1. Objectives

- Build a scaled adder that one inverting input with  $R_1$  will be amplified by 10 and the other  $R_2$  by 5.
- Use 10 kOhm resistor for one of the input resistors,  $R_1$  and calculate  $R_f$ . Use the same  $R_f$  to calculate  $R_2$ .
- Show your design in using Multisim in your pre-lab.
- Prepare a table for measurement in advance to prove that your circuit work by comparing your calculated values with the actual values.

### 3. Theory and Calculation

## 2. Theory and Calculation

### 2.1 Theory

- A scaling adder has two or more inputs with each input having a different gain. The output represents the negative scaled sum of the inputs.

### 2.2 Design and Calculation

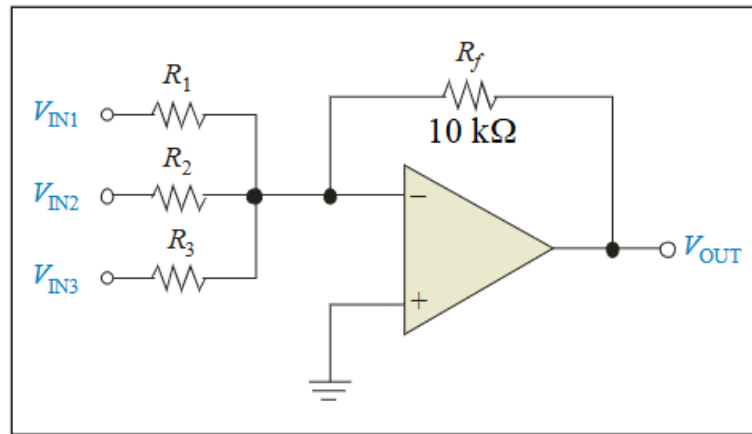


Figure 2-1: Scale Adder's design

For this design the following equipment are use:

- Resistor  $10\text{ k}\Omega$ , Resistor  $22\text{ k}\Omega$  and Resistor  $100\text{ k}\Omega$
- IC LM348N
- Function Generator
- Power Supply

Formula to calculate gain:

$$A_i = -\frac{R_f}{R_i}$$

Formula to calculate  $V_{out}$ :

$$V_{out} = \sum_{i=1}^{\infty} A_i \times V_{in_i}$$

#### - Calculation for $R_f$ :

The requirement stated that it need the gain of 10 for input 1 and gain 2 for input 2, with  $R_1 = 10\text{ k}\Omega$ :

$$A_1 = -\frac{R_f}{R_1}$$

$$-10 = -\frac{R_f}{10\text{ k}\Omega}$$

$$R_f = 100\text{ k}\Omega$$

## 2. Theory and Calculation

---

### - Calculation for $R_2$ :

$$A_2 = -\frac{R_f}{R_2}$$

$$-5 = -\frac{100k\Omega}{R_1}$$

$$R_2 = 20k\Omega$$

Because the kit does not have a resistor with value  $20k\Omega$ , so instead will use  $22k\Omega$  resistor.

### - Power supply:

#### recommended operating conditions

|                           | MIN | MAX | UNIT |
|---------------------------|-----|-----|------|
| Supply voltage, $V_{CC+}$ | 4   | 18  | V    |
| Supply voltage, $V_{CC-}$ | -4  | -18 | V    |

Figure 2-2: LM348N's datasheet

From the datasheet, it said that it recommended that the power supply of  $V_{cc+}$  should be in range from 4V to 18V, and for  $V_{cc-}$  should be from -4 to -18.

### 3. Design and Result

### 3. Design and Result

For this assignment, 6 cases will be tested, 3 will be with DC power and 3 will be from AC power.

#### 3.1 Multisim's design.

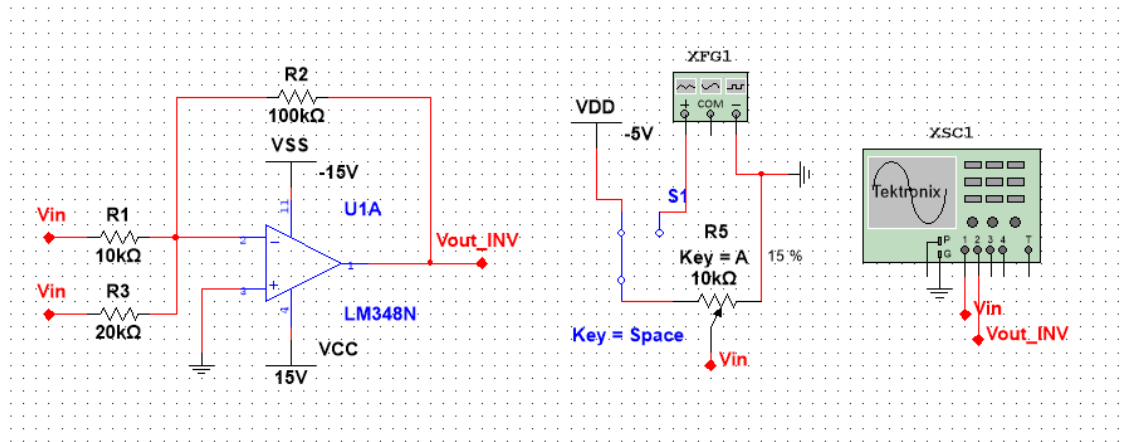


Figure 3-1: Multisim's design

#### 3.2 Breadboard's design

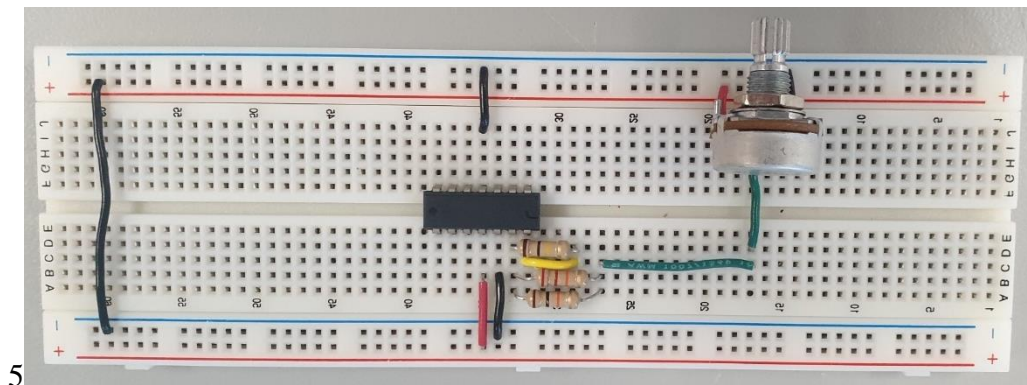


Figure 3-2: Breadboard's design

3. Result

3.3 Result

3.3.1 DC power

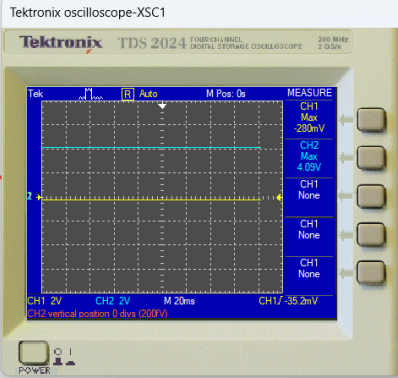
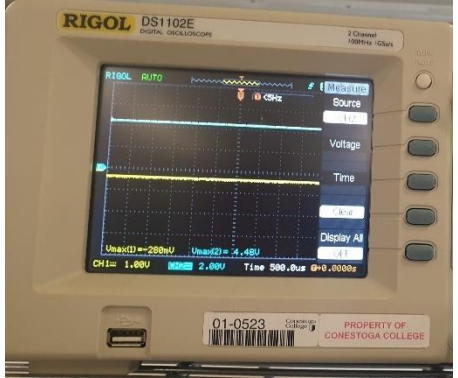
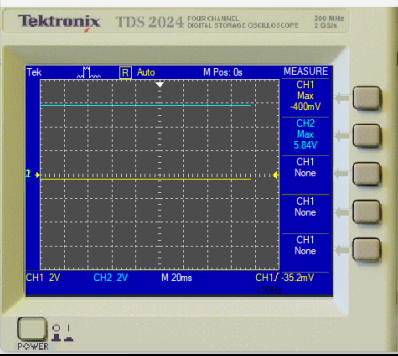
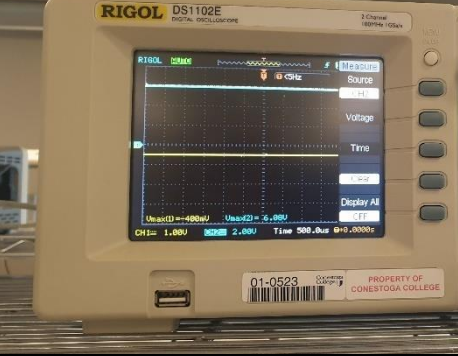
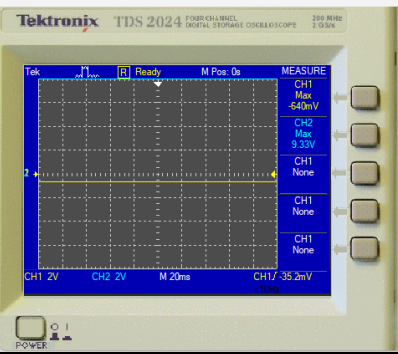
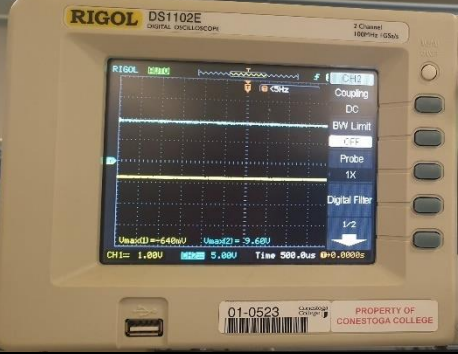
| Input | Output |                                                                                     |                                                                                       |
|-------|--------|-------------------------------------------------------------------------------------|---------------------------------------------------------------------------------------|
|       | Theory | Multisim                                                                            | Breadboard                                                                            |
| -0.28 | 4.2    |    |    |
| -0.4  | 6      |   |   |
| -0.64 | 9.6    |  |  |

Table 3-1: DC power for Scale Adder



3. Result

3.3.2 AC power

- Inverting

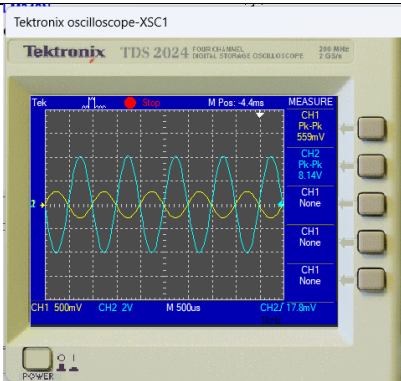
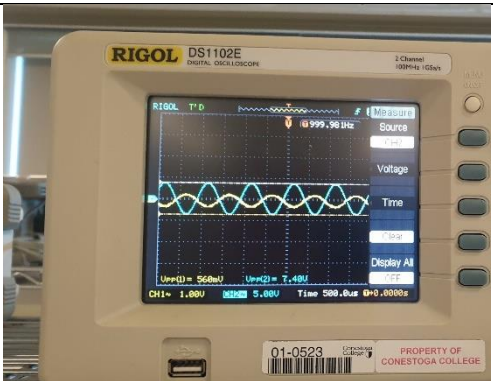
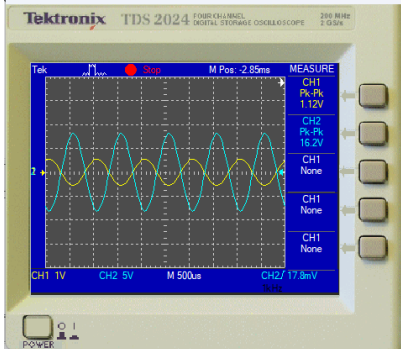
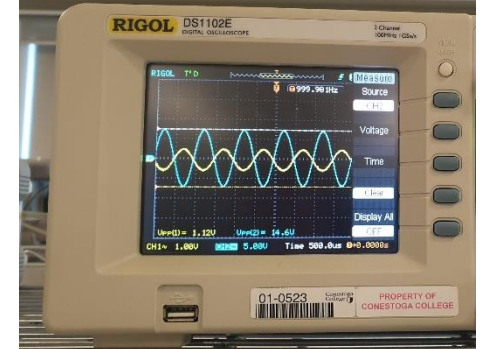
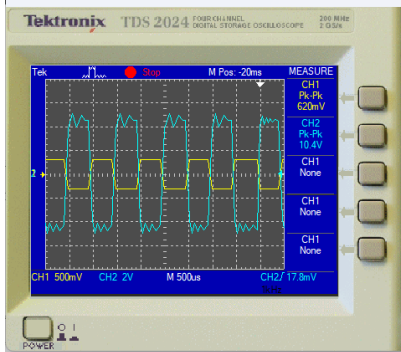

| Input<br>(Vpp) | Output |                                                                                     |                                                                                      |
|----------------|--------|-------------------------------------------------------------------------------------|--------------------------------------------------------------------------------------|
|                | Theory | Multisim                                                                            | Breadboard                                                                           |
| 0.56           | 7.4    |    |    |
| 1.12           | 16.8   |   |   |
| 0.62           | 9.3    |  |  |

Table 3-2: AC power for Scale Adder

## 4. Conclusion

---

### 4. CONCLUSION

From the result of all cases:

- All cases have Theory's result, Multisim's result and Breadboard's result nearly the same.

REFERENCES