

# LAB NOTE

**Subject: Digital Design Principles**

**Topic: Counters**

**Student: Minh Quan Tran**

**July 12<sup>th</sup>, 2024**

# Table of Contents

<b>1. Objectives .....</b>	<b>4</b>
<b>2. Theory and Design.....</b>	<b>6</b>
2.1 Theory .....	6
2.1.1 Ring Counter .....	6
2.1.2 Johnson Counter .....	6
2.2 Requirement .....	6
2.3 Solution .....	6
<b>3. VHDL and Verilog .....</b>	<b>6</b>
3.1 VHDL code .....	6
3.1.1 Top entity .....	6
3.1.2 Component Ring Counter.....	8
3.1.3 Component Ring Counter.....	9
3.2 Verilog code .....	10
3.2.1 Top Module .....	10
3.2.2 Module Timer.....	13
<b>4. Pin Planner.....</b>	<b>15</b>
4.1 Input and Output.....	15
<b>5. Result .....</b>	<b>17</b>

## TABLE OF FIGURES

Figure 2-1: Counters's Truth Table.....	6
Figure 4-1: SCEMA5F31C6N board .....	15
Figure 4-2: SW0 and SW1 Pin No .....	16
Figure 4-3: LEDR0's Pin No .....	16
Figure 4-4: HEX's Pin No .....	16
Figure 5-1: When input = '000' .....	17
Figure 5-2: When input = '111' .....	17
Figure 5-3: When input '101' .....	18
Figure 5-4: Input '101' with Complement mode .....	18
Figure 5-5: Input '101' with Multiline mode .....	19
Figure 5-6: Result for adding them up .....	19

## 1. Objectives

---

### 1. Objectives

- Design a Counters using Quartus software.
- Write a VHDL and Verilog code from the design.
- Push the code and run to the SCEMA5F31C6N board.

## 2. Theory and Design

### 2.1 Theory

#### 2.1.1 Ring Counter

A ring counter is a type of counter composed of a circular shift register, where the output of the last flip-flop is fed back to the input of the first flip-flop. In a ring counter, only one flip-flop is set to '1' (or 'high') at any time, and this '1' circulates around the ring. For an N-bit ring counter, the sequence repeats every N states. This type of counter is simple but has limited use due to the fixed number of states equal to the number of flip-flops.

#### 2.1.2 Johnson Counter

A Johnson counter, also known as a twisted ring counter or Möbius counter, is a modified version of the ring counter. In a Johnson counter, the complement of the output of the last flip-flop is fed back to the input of the first flip-flop. This configuration creates a sequence of states that is twice the number of flip-flops, effectively doubling the counting states compared to a standard ring counter. For an N-bit Johnson counter, the sequence repeats every 2N states, making it more efficient in terms of state utilization.

### 2.2 Requirement

- Use VHDL and Verilog to implement a Counters and display to LED [0:7].
- Introduction to the VHDL Case statement.
- **Above and beyond:** Adding Complement mode

### 2.3 Solution

To design this system, first need to identify input and output:

- Input will be from BTN0 to BTN3
- Output will be LED[8:0].

Then identify what the output will be, from the 2 inputs,

Straight ring/Overbeck counter					Twisted ring/Johnson counter				
State	Q0	Q1	Q2	Q3	State	Q0	Q1	Q2	Q3
0	1	0	0	0	0	0	0	0	0
1	0	1	0	0	1	1	0	0	0
2	0	0	1	0	2	1	1	0	0
3	0	0	0	1	3	1	1	1	0
0	1	0	0	0	4	1	1	1	1
1	0	1	0	0	5	0	1	1	1
2	0	0	1	0	6	0	0	1	1
3	0	0	0	1	7	0	0	0	1
0	1	0	0	0	0	0	0	0	0

Figure 2-1: Counters's Truth Table

### 3. VHDL and Verilog

#### 3.1 VHDL code

##### 3.1.1 Top entity

```
library ieee;
use ieee.std_logic_1164.ALL;

entity MTran_Lab8_VHDL_Counters is
port
(
    -- Inputs
    BTN          : in std_logic;
    Reset        : in std_logic;
    Complement    : in std_logic;

    -- Outputs
    LED_Ring      : out std_logic_vector (3 downto 0);
    LED_Johnson   : out std_logic_vector (3 downto 0);

    HEX0          : out std_logic_vector (6 downto 0);
    HEX4          : out std_logic_vector (6 downto 0)
);
end entity;

architecture Behavioral of MTran_Lab8_VHDL_Counters is

--Signal Declaration
signal state: integer:= 0;

signal RingCounterState : integer := 0;
signal JohnsonCounterState: integer := 0;

-- Module Declaration
component MTran_Lab8_VHDL_RingCounter is
port
(
    -- Inputs
    CLK          : in std_logic;
    Reset        : in std_logic;
    Complement    : in std_logic;

    -- Outputs
    Q             : out std_logic_vector (3 downto 0);
    stateNumber : out integer
);
end component;

component MTran_Lab8_VHDL_JohnsonCounter is
port
(
    -- Inputs
    CLK          : in std_logic;
    Reset        : in std_logic;
    Complement    : in std_logic;

    -- Outputs
    Q             : out std_logic_vector (3 downto 0);
    stateNumber : out integer
```

### 3. VHDL and Verilog

```
);  
end component;  
  
-- Function declaration  
function SevenSegmentDisplay (Number : integer) return std_logic_vector is  
begin  
    case (Number) is  
        when 0      => return "1000000";  
        when 1      => return "1111001";  
        when 2      => return "0100100";  
        when 3      => return "0110000";  
        when 4      => return "0011001";  
        when 5      => return "0010010";  
        when 6      => return "0000010";  
        when 7      => return "1111000";  
        when 8      => return "0000000";  
        when 9      => return "0010000";  
        when others => return "1111111";  
    end case;  
end SevenSegmentDisplay;  
  
begin  
    -- Module Instantiate  
    module_RingCounter: MTran_Lab8_VHDL_RingCounter  
    port map  
    (  
        -- Inputs  
        CLK      => BTN ,  
        Reset    => Reset,  
        Complement => Complement,  
  
        -- Output  
        Q          => LED_Ring,  
        stateNumber => RingCounterState  
    );  
  
    module_JohnsonCounter: MTran_Lab8_VHDL_JohnsonCounter  
    port map  
    (  
        -- Inputs  
        CLK      => BTN ,  
        Reset    => Reset,  
        Complement => Complement,  
  
        -- Output  
        Q          => LED_Johnson,  
        stateNumber => JohnsonCounterState  
    );  
  
    -- Process  
    process(RingCounterState, JohnsonCounterState) is  
    begin  
        HEX0 <= SevenSegmentDisplay(RingCounterState);  
        HEX4 <= SevenSegmentDisplay(JohnsonCounterState);  
    end process;  
  
end Behavioral;
```

### 3. VHDL and Verilog

#### 3.1.2 Component Ring Counter

```
library ieee;
use ieee.std_logic_1164.all;

entity MTran_Lab8_VHDL_RingCounter is
port
(
    -- Inputs
    CLK          : in    std_logic;
    Reset        : in    std_logic;
    Complement    : in    std_logic;

    -- Outputs
    Q             : out   std_logic_vector (3 downto 0);
    stateNumber   : out   integer
);
end entity;

architecture RTL of MTran_Lab8_VHDL_RingCounter is
-- Signal Declaration
signal state          : integer      := 0;
signal complementMode : std_logic := '0';

signal Output          : std_logic_vector (3 downto 0) := "0000";

-- Procedure
procedure Increment (signal Counter: inout integer) is
begin
    if Counter < 3 then
        Counter <= Counter + 1;
    else
        Counter <= 0;
    end if;
end procedure;

-- Main code
begin

    -- Process
    process (CLK, Reset)
    begin
        if Reset = '0' then
            state <= 0;
        else
            if rising_edge(CLK) then
                Increment(state);
            end if;
        end if;
    end process;

    process (state, complementMode)
    begin
        case (state) is
            when 0      => Output <= "1000";
            when 1      => Output <= "0100";
            when 2      => Output <= "0010";
            when 3      => Output <= "0001";
            when others => Output <= "0000";
        end case;
    end process;
end architecture;
```



### 3. VHDL and Verilog

```
        stateNumber <= state;
    end process;

    -- Check BTN1 for complement mode
    process (Complement)
    begin
        if rising_edge(Complement) then
            complementMode <= not complementMode;
        end if;
    end process;

    -- Process complement mode
    process (complementMode) is
    begin
        if complementMode = '1' then
            Q <= not Output;
        else
            Q <= Output;
        end if;
    end process;

end RTL;
```

#### 3.1.3 Component Ring Counter

```
library ieee;
use ieee.std_logic_1164.all;

entity MTran_Lab8_VHDL_JohnsonCounter is
port
(
    -- Inputs
    CLK          : in    std_logic;
    Reset        : in    std_logic;
    Complement    : in    std_logic;

    -- Outputs
    Q             : out   std_logic_vector (3 downto 0);
    stateNumber   : out   integer
);
end entity;

architecture RTL of MTran_Lab8_VHDL_JohnsonCounter is
    -- Signal Declaration
    signal state      : integer      := 0;
    signal complementMode : std_logic := '0';

    signal Output      : std_logic_vector (3 downto 0) := "0000";

    -- Procedure
    procedure Increment (signal Counter: inout integer) is
    begin
        if Counter < 7 then
            Counter <= Counter + 1;
        else
            Counter <= 0;
        end if;
    end procedure;

    -- Main code
```

### 3. VHDL and Verilog

```
begin

    -- Process
    process (CLK, Reset)
    begin
        if Reset = '0' then
            state <= 0;
        else
            if rising_edge(CLK) then
                Increment(State);
            end if;
        end if;
    end process;

    process (state, complementMode)
    begin
        case (state) is
            when 0      => Output <= "0000";
            when 1      => Output <= "1000";
            when 2      => Output <= "1100";
            when 3      => Output <= "1110";
            when 4      => Output <= "1111";
            when 5      => Output <= "0111";
            when 6      => Output <= "0011";
            when 7      => Output <= "0001";
            when others => Output <= "0000";
        end case;

        stateNumber <= state;
    end process;

    -- Check BTN1 for complement mode
    process (Complement)
    begin
        if rising_edge(Complement) then
            complementMode <= not complementMode;
        end if;
    end process;

    -- Process complement mode
    process (complementMode) is
    begin
        if complementMode = '1' then
            Q <= not Output;
        else
            Q <= Output;
        end if;
    end process;

end RTL;
```

## 3.2 Verilog code

### 3.2.1 Top Module

```
module MTran_Lab7_Verilog_MagnitudeComparator
(
    input wire CLOCK_50,
    input wire [3:0] A,
    input wire [3:0] B,
    input mode,
    input speed,
```

### 3. VHDL and Verilog

---

```
    output reg [2:0] LED,
    output reg [6:0] HEX0,
    output reg [6:0] HEX1,
    output reg [6:0] HEX2,
    output reg [6:0] HEX3,
    output reg [6:0] HEX4,
    output reg [6:0] HEX5
);

// Signals declaration
reg [31:0] intA;
reg [31:0] intB;

reg Enable;

wire [31:0] Seconds1;
wire [31:0] Minutes1;
wire [31:0] Hours1;

wire [31:0] Seconds2;
wire [31:0] Minutes2;
wire [31:0] Hours2;

// Module Instantiation
MTran_Lab7_Verilog_Timer
#(
    .MAXSECONDS(60),
    .MAXMINUTES(60),
    .MAXHOURS(24),
    .CLKFREQUENCY(500000) // 500kHz => Clock 10 times faster
)

Tim1
(
    .Clk(CLOCK_50),
    .Enable(Enable),
    .Seconds(Seconds1),
    .Minutes(Minutes1),
    .Hours(Hours1)
);

MTran_Lab7_Verilog_Timer
#(
    .MAXSECONDS(60),
    .MAXMINUTES(60),
    .MAXHOURS(24),
    .CLKFREQUENCY(50000000) // 50 MHz => Normal Clk
)

Tim2
(
    .Clk(CLOCK_50),
    .Enable(Enable),
    .Seconds(Seconds2),
    .Minutes(Minutes2),
    .Hours(Hours2)
);

// Function for Seven Segment Display
function [6:0] SevenSegmentDisplay;
    input [3:0] Number;
    begin
        case (Number)
```

### 3. VHDL and Verilog

```
        4'h0: SevenSegmentDisplay = 7'b1000000;
        4'h1: SevenSegmentDisplay = 7'b1111001;
        4'h2: SevenSegmentDisplay = 7'b0100100;
        4'h3: SevenSegmentDisplay = 7'b0110000;
        4'h4: SevenSegmentDisplay = 7'b0011001;
        4'h5: SevenSegmentDisplay = 7'b0010010;
        4'h6: SevenSegmentDisplay = 7'b0000010;
        4'h7: SevenSegmentDisplay = 7'b1111000;
        4'h8: SevenSegmentDisplay = 7'b0000000;
        4'h9: SevenSegmentDisplay = 7'b0010000;
        default: SevenSegmentDisplay = 7'b1111111;
    endcase
end
endfunction

always @(posedge CLOCK_50)
begin
    if (mode == 1'b0)
        begin
            // Disable Timer
            Enable = 1'b0;

            // Reset HEX2
            HEX2 = 7'b1111111;

            // Convert A and B from std_logic to integer
            intA = A;
            intB = B;

            // Display A and B in decimal
            // A
            HEX0 = SevenSegmentDisplay(intA % 10);
            HEX1 = SevenSegmentDisplay(intA / 10);

            // B
            HEX4 = SevenSegmentDisplay(intB % 10);
            HEX5 = SevenSegmentDisplay(intB / 10);

            // Compare A and B
            if (intA > intB)
                begin
                    LED = 3'b100;
                    HEX3 = 7'b0100111;
                end
            else if (intA == intB)
                begin
                    LED = 3'b010;
                    HEX3 = 7'b0110111;
                end
            else
                begin
                    LED = 3'b001;
                    HEX3 = 7'b0110011;
                end
            end
        end
    else
        begin
            Enable = 1'b1;
            LED = 3'b000;
        end
    end
end
```

### 3. VHDL and Verilog

```
    if (speed == 1'b0) //normal mode
    begin
        // Display Second
        HEX0  = SevenSegmentDisplay(Seconds2 % 10);
        HEX1  = SevenSegmentDisplay(Seconds2 / 10);

        // Display Minute
        HEX2  = SevenSegmentDisplay(Minutes2 % 10);
        HEX3  = SevenSegmentDisplay(Minutes2 / 10);

        // Display Hour
        HEX4  = SevenSegmentDisplay(Hours2 % 10);
        HEX5  = SevenSegmentDisplay(Hours2 / 10);
    end
    else if (speed == 1'b1)
    begin
        // Display Second
        HEX0  = SevenSegmentDisplay(Seconds1 % 10);
        HEX1  = SevenSegmentDisplay(Seconds1 / 10);

        // Display Minute
        HEX2  = SevenSegmentDisplay(Minutes1 % 10);
        HEX3  = SevenSegmentDisplay(Minutes1 / 10);

        // Display Hour
        HEX4  = SevenSegmentDisplay(Hours1 % 10);
        HEX5  = SevenSegmentDisplay(Hours1 / 10);
    end
end
end
endmodule
```

#### 3.2.2 Module Timer

```
module MTran_Lab7_Verilog_Timer

#(
parameter MAXSECONDS      = 60,
parameter MAXMINUTES     = 60,
parameter MAXHOURS       = 24,
parameter CLKFREQUENCY    = 50000000
)

(
    input wire Clk,
    input wire Enable,
    inout reg [31:0] Seconds,
    inout reg [31:0] Minutes,
    inout reg [31:0] Hours
);

// Signal Declaration
reg [31:0] Ticks = 0;

// Main Logic
always @(posedge Clk)
begin
    if (Enable)
    begin
        // Increment Ticks
```

### 3. VHDL and Verilog

---

```
Ticks = Ticks + 1;
  if (Ticks == CLKFREQUENCY - 1)
    begin
      Ticks    = 0;
      Seconds  = Seconds + 1;
    end

  if (Seconds == MAXSECONDS)
    begin
      Seconds = 0;
      Minutes = Minutes + 1;
    end

  if (Minutes == MAXMINUTES)
    begin
      Minutes = 0;
      Hours   = Hours + 1;
    end

  if (Hours == MAXHOURS)
    begin
      Hours   = 0;
    end
  end
end
endmodule
```

### 4. Pin Planner

#### 4.1 Input and Output

 


Figure 4-1: SCEMA5F31C6N board

Assigning:

SW[0]: SW0  
SW[1]: SW1  
SW[2]: SW2

Mode[0]: SW7  
Mode[1]: SW8  
EN: SW9

LED[0]: LEDR0  
LED[1]: LEDR1  
LED[2]: LEDR2  
LED[3]: LEDR3  
LED[4]: LEDR4  
LED[5]: LEDR5  
LED[6]: LEDR6  
LED[7]: LEDR7

HEX0[0]: HEX0[0]  
HEX0[1]: HEX0[1]  
HEX0[2]: HEX0[2]  
HEX0[3]: HEX0[3]  
HEX0[4]: HEX0[4]  
HEX0[5]: HEX0[5]  
HEX0[6]: HEX0[6]

## 4. Pin Planner

From the DE1\_SoC\_User\_Manual,

<i>Signal Name</i>	<i>FPGA Pin No.</i>	<i>Description</i>	<i>I/O Standard</i>
SW[0]	PIN_AB12	Slide Switch[0]	3.3V
SW[1]	PIN_AC12	Slide Switch[1]	3.3V
SW[2]	PIN_AF9	Slide Switch[2]	3.3V
SW[3]	PIN_AF10	Slide Switch[3]	3.3V
SW[4]	PIN_AD11	Slide Switch[4]	3.3V
SW[5]	PIN_AD12	Slide Switch[5]	3.3V

Figure 4-2: SW0 and SW1 Pin No

<i>Signal Name</i>	<i>FPGA Pin No.</i>	<i>Description</i>	<i>I/O Standard</i>
LEDR[0]	PIN_V16	LED [0]	3.3V
LEDR[1]	PIN_W16	LED [1]	3.3V

Figure 4-3: LEDR0's Pin No

<i>Signal Name</i>	<i>FPGA Pin No.</i>	<i>Description</i>	<i>I/O Standard</i>
HEX0[0]	PIN_AE26	Seven Segment Digit 0[0]	3.3V
HEX0[1]	PIN_AE27	Seven Segment Digit 0[1]	3.3V
HEX0[2]	PIN_AE28	Seven Segment Digit 0[2]	3.3V
HEX0[3]	PIN_AG27	Seven Segment Digit 0[3]	3.3V
HEX0[4]	PIN_AF28	Seven Segment Digit 0[4]	3.3V
HEX0[5]	PIN_AG28	Seven Segment Digit 0[5]	3.3V
HEX0[6]	PIN_AH28	Seven Segment Digit 0[6]	3.3V

Figure 4-4: HEX's Pin No



## 5. Result

 


Figure 5-1: When input = '000'.

$SW2 = 0$ ,  $SW1 = 0$ ,  $SW0 = 0$  which should be 0, **LED0** asserted and the 7 segment LED displaying **0**.

 


Figure 5-2: When input = '111'

$SW2 = 1$ ,  $SW1 = 1$ ,  $SW0 = 1$  which should be 7, **LED7** asserted and the 7 segment LED displaying **7**.

## 5. Result

 


Figure 5-3: When input '101'

SW2 = 1, SW1 = 0, SW0 = 1 which should be 5, **LED5** asserted and the 7 segment LED displaying 5.

Different mode:

- Complement mode:

 


Figure 5-4: Input '101' with Complement mode

In this mode, rather than LED5 assert, all other LED except LED5 asserted. To activate this mode SW [8:7] = '01'.



## 5. Result

### - Multiline Mode:

 


Figure 5-5: Input '101' with Multiline mode

In this mode, when input is '101' which is 5, LED0 to LED5 lit up. To activate this mode SW [8:7] = '10'.

### - Complement Multiline Mode:

 


Figure 5-6: Result for adding them up

In this mode, it take the output of Multiline Mode and complemented it. To activate this mode SW [8:7] = '11'

REFERENCES