

# **LAB NOTE**

**Subject: Electronic Design Principles**

**Topic: Astable Multivibrator**

**Student: Minh Quan Tran**

**May , 2024**

# Table of Contents

<b>1. Objectives.....</b>	<b>4</b>
<b>2. Theory and Design.....</b>	<b>5</b>
2.1 Theory .....	5
2.2 Design and Calculation .....	5
<b>3. Result .....</b>	<b>6</b>
3.1 16 Hz .....	6
3.1.1 Calculation for equipment .....	6
3.1.2 Multisim Design .....	6
3.1.3 Breadboard Design .....	7
3.1.4 Result.....	8
3.2 33 Hz .....	9
3.2.1 Calculation for equipment .....	9
3.2.2 Multisim Design .....	9
3.2.3 Breadboard Design .....	10
3.2.4 Result.....	11
3.3 80 Hz .....	12
3.3.1 Calculation for equipment .....	12
3.3.2 Multisim Design .....	12
3.3.3 Breadboard Design .....	13
3.3.4 Result.....	14
3.4 5 Hz .....	15
3.4.1 Calculation for equipment .....	15
3.4.2 Multisim Design .....	15
3.4.3 Breadboard Design .....	16
3.4.4 Result.....	17
3.5 20 Hz (67% ON and 33% OFF) .....	18
3.5.1 Calculation for equipment .....	18
3.5.2 Multisim Design .....	18
3.5.3 Breadboard Design .....	20
3.5.4 Result.....	21
<b>4. CONCLUSION.....</b>	<b>22</b>

## TABLE OF FIGURES

Figure 2-1: Astable Multivibrator Circuit .....	5
Figure 3-1: Circuit design with $R = 47k\Omega$ and $C = 1\mu F$ .....	6
Figure 3-2: Circuit's output for 16 Hz .....	7
Figure 3-3: Breadboard's design for 16 Hz .....	7
Figure 3-4: Breadboard's output for 16 Hz.....	8
Figure 3-5: Circuit design with $R = 22k\Omega$ and $C = 1\mu F$ .....	9
Figure 3-6: Circuit's output for 33 Hz .....	10
Figure 3-7: Breadboard's design for 33 Hz .....	10
Figure 3-8: Breadboard's output for 33 Hz.....	11
Figure 3-9: Circuit design with $R_2 = 10k\Omega$ and $C_2 = 1\mu F$ .....	12
Figure 3-10: Circuit's output for 80 Hz .....	13
Figure 3-11: Breadboard's design for 80 Hz .....	13
Figure 3-12: Breadboard's output for 80 Hz.....	14
Figure 3-13: Circuit design with $R_2 = 220k\Omega$ and $C_2 = 1\mu F$ .....	15
Figure 3-14: Circuit's output for 5 Hz .....	16
Figure 3-15: Breadboard's design for 5 Hz .....	16
Figure 3-16: Breadboard's output for 5 Hz.....	17
Figure 3-17: Circuit design with $R_2 = 47k\Omega$ , $C_2 = 1\mu F$ and $R_3 = 22k\Omega$ , $C_1 = 1\mu F$ .....	18
Figure 3-18: Circuit's output of Chanel 1 for 20Hz (67% ON, 33% OFF time) .....	18
Figure 3-19: Circuit's output of Chanel 2 for 20Hz (33% ON, 67% OFF) .....	19
Figure 3-20: Breadboard's design for 20 Hz .....	20
Figure 3-21: Breadboard's output for 20Hz (Channel 1).....	20
Figure 3-22: Breadboard's output for 20Hz (Channel 2).....	21

~~~~~

## TABLE'S OF TABLE

|                                  |    |
|----------------------------------|----|
| Table 3-1: Result for 16 Hz..... | 8  |
| Table 3-2: Result for 33 Hz..... | 11 |
| Table 3-3: Result for 80 Hz..... | 14 |
| Table 3-4: Result for 5 Hz.....  | 17 |
| Table 3-5: Result for 20 Hz..... | 21 |

## **1. Objectives**

---

### **1. Objectives**

To create a working Astable Multivibrator using 2 BJTs, LEDs and capacitors.

Step 1: Design and calculate the equipment in the circuit.

Step 2: Simulate the result in Multisim to test the theory.

Step 3: Build the circuit based on theory and Multisim design.

## 2. Theory and Design

### 2. Theory and Design

#### 2.1 Theory

Astable-Multivibrator basically is used to generate the square waves at a desired frequency without any external intervention.

#### 2.2 Design and Calculation

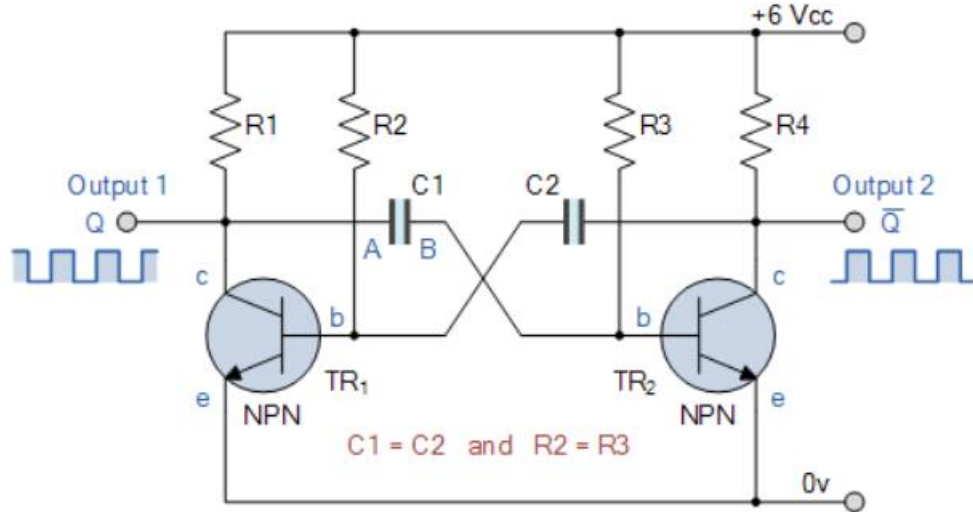


Figure 2-1: Astable Multivibrator Circuit

For this design the following equipment are use:

- 4 Resistor
- 2 Capacitor
- 2 BJT Transistors
- Power Supply

Astable Multivibrator's Periodic time (for Output 1):

$$\begin{cases} T = t_1 + t_2 \\ t_1 = \ln(2) \times R_2 \times C_2 \\ t_2 = \ln(2) \times R_3 \times C_1 \end{cases} \quad (2.1)$$

*Equation 2-1: Astable Multivibrator's Periodic time formula*

For this assignment, 5 sample frequencies will be tested.

### 3. Result

## 3. Result

### 3.1 16 Hz

#### 3.1.1 Calculation for equipment

Because  $R_2 = R_3$  and  $C_1 = C_2$  so,

$$t_1 = t_2 = \ln(2) \times R_2 \times C_2$$

To design an Astable Multivibrator with frequency of 16Hz, the periodic time will be:

$$T = \frac{1}{f} = \frac{1}{16 \text{ Hz}} = 62.5 \text{ (ms)}$$

So  $t_1$  and  $t_2$  will be.

$$T = t_1 + t_2 = 2 \times t_1$$

$$t_1 = \frac{T}{2} = 31.25 \text{ (ms)}$$

From the result, choosing  $R_2 = 47k\Omega$  and  $C_2 = 1\mu F$  will give the closest time:

$$t_1 = \ln(2) \times R_2 \times C_2 = 32.5 \text{ (ms)}$$

$$f = \frac{1}{T} = \frac{1}{2 \times t_1} = 15.38 \text{ (Hz)}$$

#### 3.1.2 Multisim Design

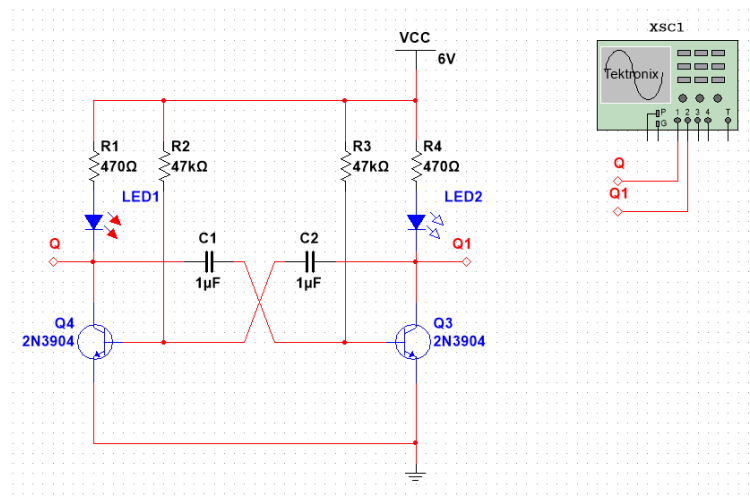


Figure 3-1: Circuit design with  $R = 47k\Omega$  and  $C = 1\mu F$

3. Result

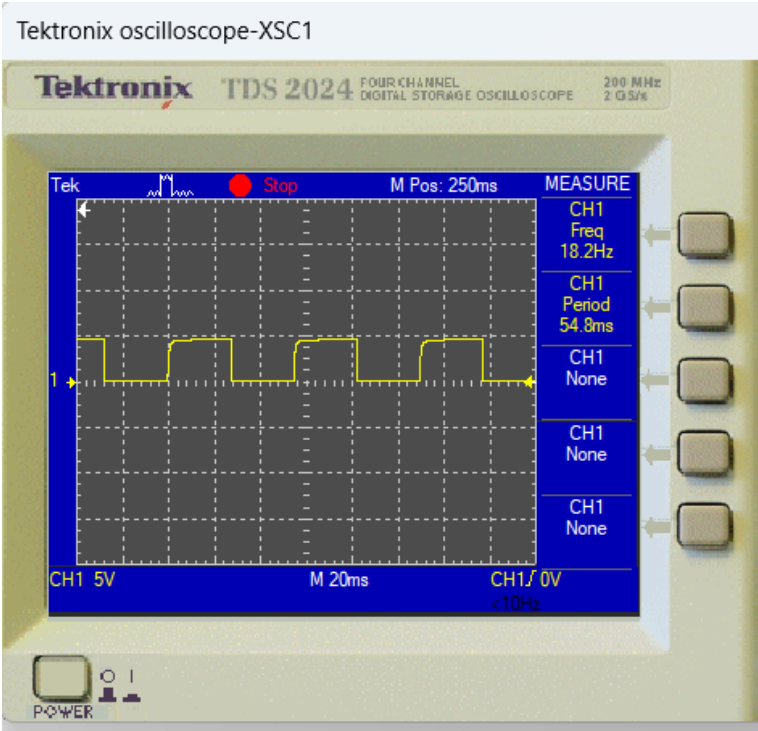


Figure 3-2: Circuit's output for 16 Hz

3.1.3 Breadboard Design

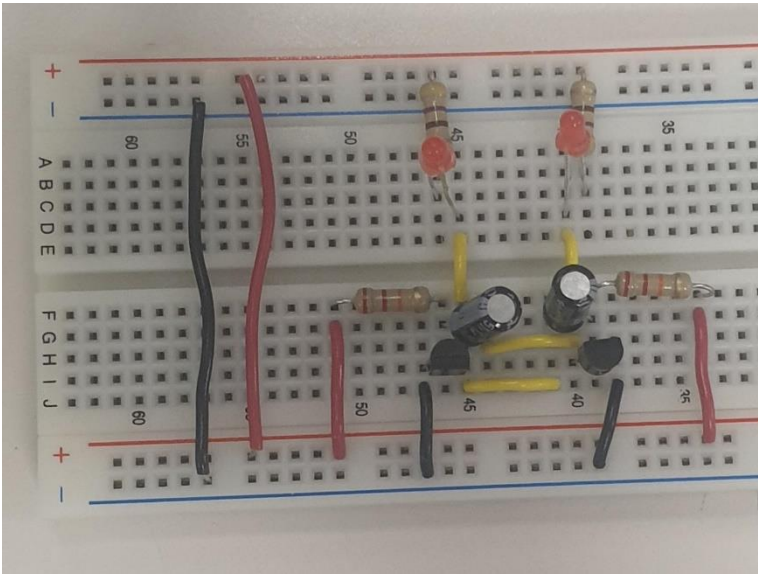


Figure 3-3: Breadboard's design for 16 Hz

3. Result

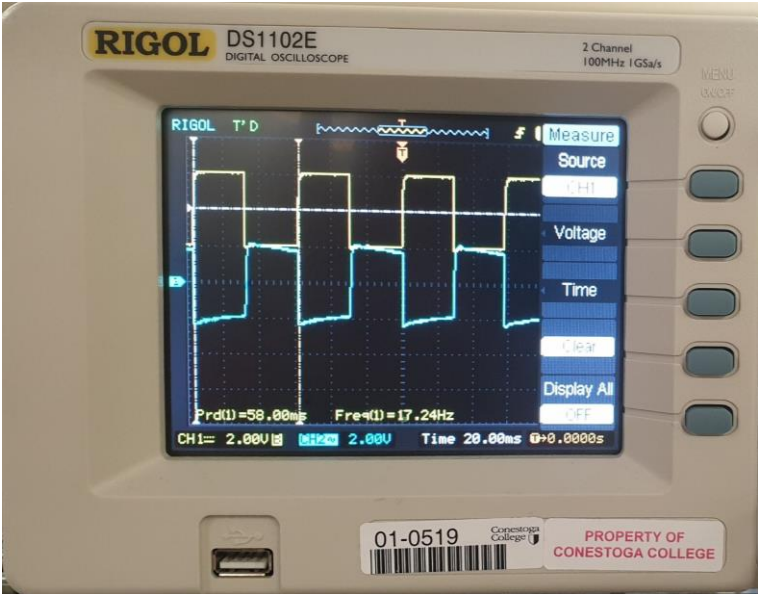


Figure 3-4: Breadboard's output for 16 Hz

3.1.4 Result

| Theory expected frequency (Hz) | Multisim’s frequency (Hz) | Breadboard’s frequency (Hz) |
|--------------------------------|---------------------------|-----------------------------|
| 15.38Hz                        | 18.2Hz                    | 17.24Hz                     |

Table 3-1: Result for 16 Hz



### 3. Result

#### 3.2 33 Hz

##### 3.2.1 Calculation for equipment

Because  $R_2 = R_3$  and  $C_1 = C_2$  so,

$$t_1 = t_2 = \ln(2) \times R_2 \times C_2$$

To design an Astable Multivibrator with 33 Hz, the periodic time will be:

$$T = \frac{1}{f} = \frac{1}{33 \text{ Hz}} = 30.3(\text{ms})$$

So  $t_1$  and  $t_2$  will be.

$$T = t_1 + t_2 = 2 \times t_1$$
$$t_1 = \frac{T}{2} = 15.15 (\text{ms})$$

From the result, choosing  $R_2 = 22k\Omega$  and  $C_2 = 1\mu F$  will be best:

$$t_1 = \ln(2) \times R_2 \times C_2 = 15.246(\text{ms})$$

$$f = \frac{1}{T} = \frac{1}{2 \times t_1} = 32.79 (\text{Hz})$$

##### 3.2.2 Multisim Design

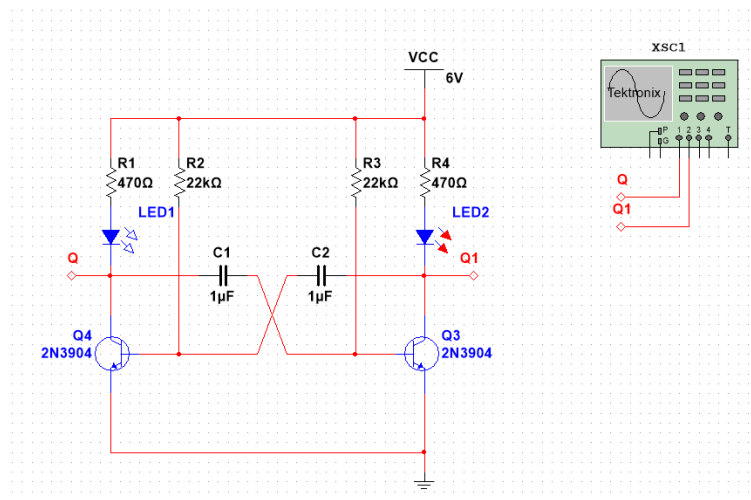


Figure 3-5: Circuit design with  $R = 22k\Omega$  and  $C = 1\mu F$

3. Result

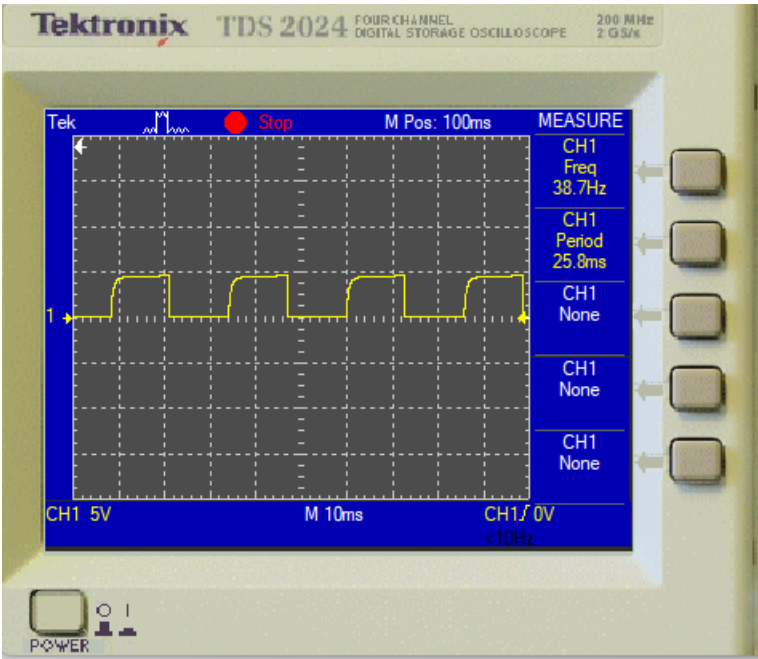


Figure 3-6: Circuit's output for 33 Hz

3.2.3 Breadboard Design

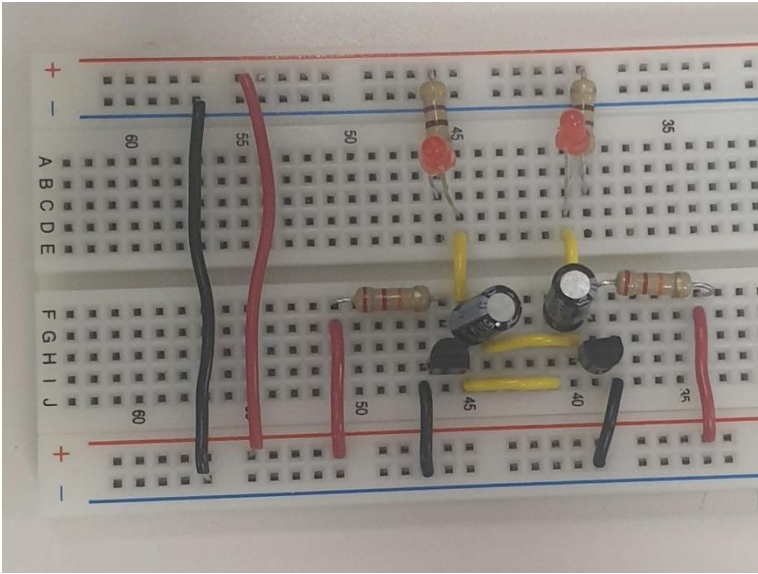


Figure 3-7: Breadboard's design for 33 Hz

3. Result

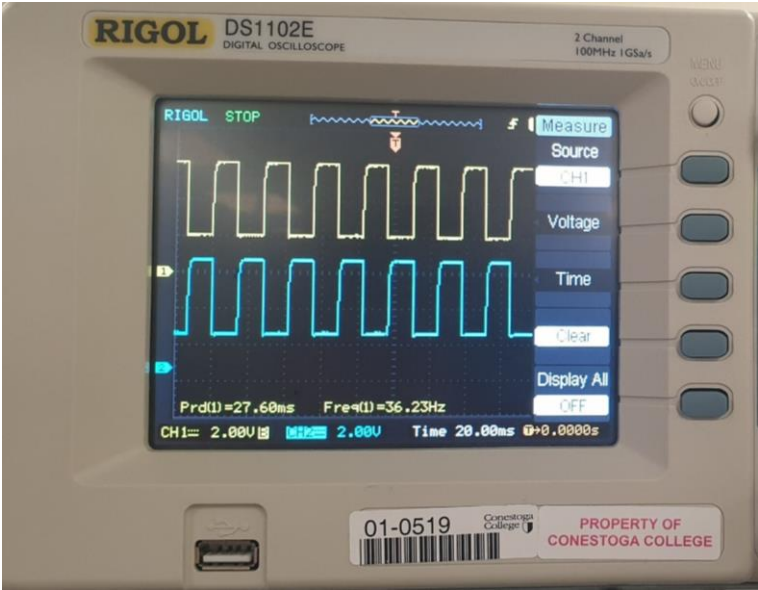


Figure 3-8: Breadboard's output for 33 Hz

3.2.4 Result

| Theory expected frequency (Hz) | Multisim expected frequency (Hz) | Breadboard expected frequency (Hz) |
|--------------------------------|----------------------------------|------------------------------------|
| 32.79 Hz                       | 38.7 Hz                          | 36.23 Hz                           |

Table 3-2: Result for 33 Hz

### 3. Result

#### 3.3 80 Hz

##### 3.3.1 Calculation for equipment

Because  $R_2 = R_3$  and  $C_1 = C_2$  so,

$$t_1 = t_2 = \ln(2) \times R_2 \times C_2$$

To design an Astable Multivibrator with 80 Hz, the periodic time will be:

$$T = \frac{1}{f} = \frac{1}{80 \text{ Hz}} = 12.5 \text{ (ms)}$$

So  $t_1$  and  $t_2$  will be.

$$T = t_1 + t_2 = 2 \times t_1$$

$$t_1 = \frac{T}{2} = 6.25 \text{ (ms)}$$

From the result, choosing  $R_2 = 10k\Omega$  and  $C_2 = 1\mu F$  will be best:

$$t_1 = \ln(2) \times R_2 \times C_2 = 6.93 \text{ (ms)}$$

$$f = \frac{1}{T} = \frac{1}{2 \times t_1} = 72.15 \text{ (Hz)}$$

##### 3.3.2 Multisim Design

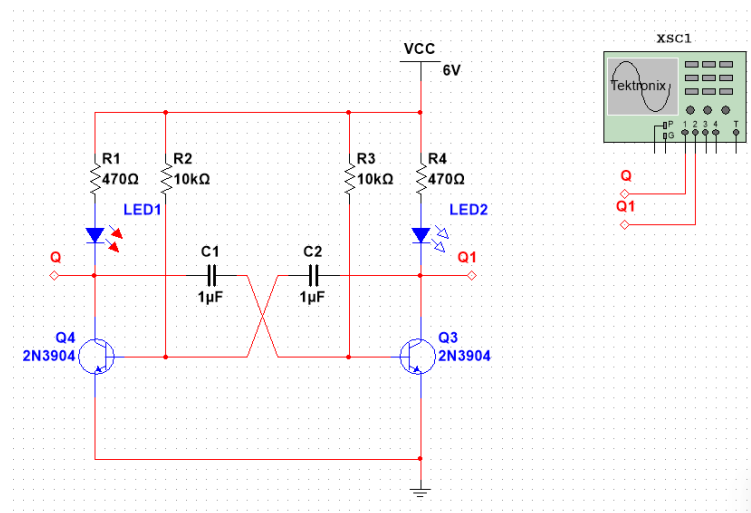


Figure 3-9: Circuit design with  $R_2 = 10k\Omega$  and  $C_2 = 1\mu F$

3. Result

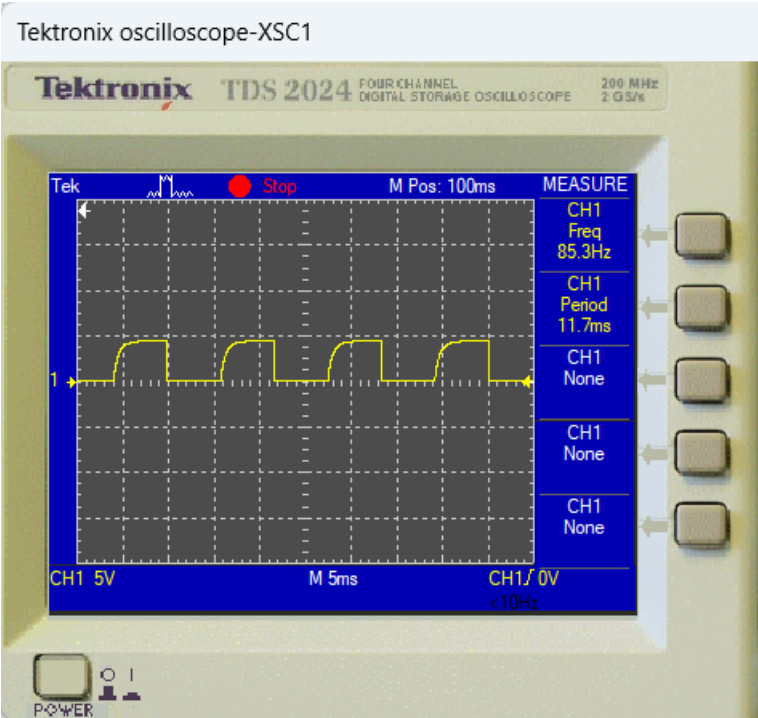


Figure 3-10: Circuit's output for 80 Hz

3.3.3 Breadboard Design

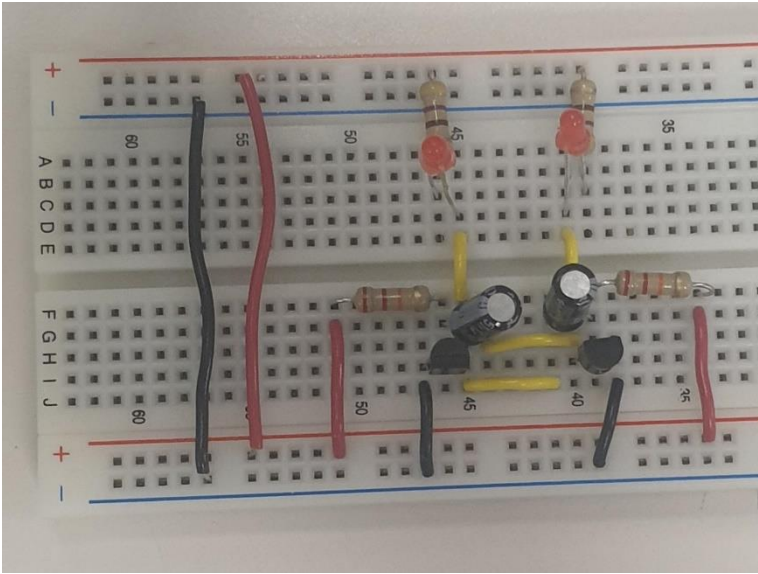


Figure 3-11: Breadboard's design for 80 Hz

3. Result

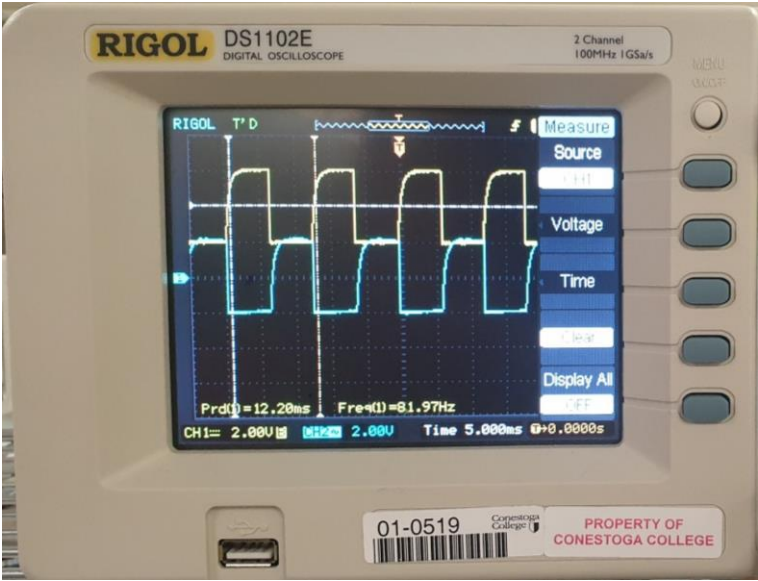


Figure 3-12: Breadboard's output for 80 Hz

3.3.4 Result

| Theory expected frequency (Hz) | Multisim expected frequency (Hz) | Breadboard expected frequency (Hz) |
|--------------------------------|----------------------------------|------------------------------------|
| 72.15 Hz                       | 85.3 Hz                          | 81.97 Hz                           |

Table 3-3: Result for 80 Hz

### 3. Result

#### 3.4 5 Hz

##### 3.4.1 Calculation for equipment

Because  $R_2 = R_3$  and  $C_1 = C_2$  so,

$$t_1 = t_2 = \ln(2) \times R_2 \times C_2$$

To design an Astable Multivibrator with 5 Hz, the periodic time will be:

$$T = \frac{1}{f} = \frac{1}{5 \text{ Hz}} = 200(\text{ms})$$

So  $t_1$  and  $t_2$  will be.

$$T = t_1 + t_2 = 2 \times t_1$$

$$t_1 = \frac{T}{2} = 100(\text{ms})$$

From the result, choosing  $R_2 = 220\text{k}\Omega$  and  $C_2 = 1\mu\text{F}$  will be best:

$$t_1 = \ln(2) \times R_2 \times C_2 = 152.46 (\text{ms})$$

$$f = \frac{1}{T} = \frac{1}{2 \times t_1} = 6.56 (\text{Hz})$$

##### 3.4.2 Multisim Design

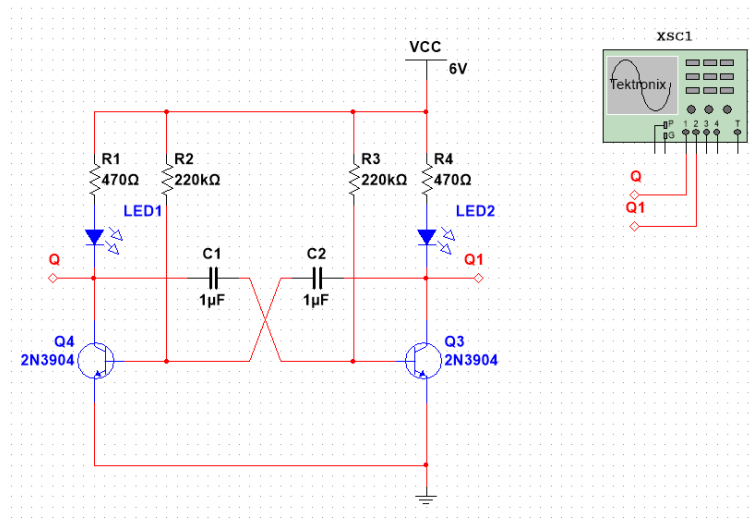


Figure 3-13: Circuit design with  $R_2 = 220\text{k}\Omega$  and  $C_2 = 1\mu\text{F}$

3. Result

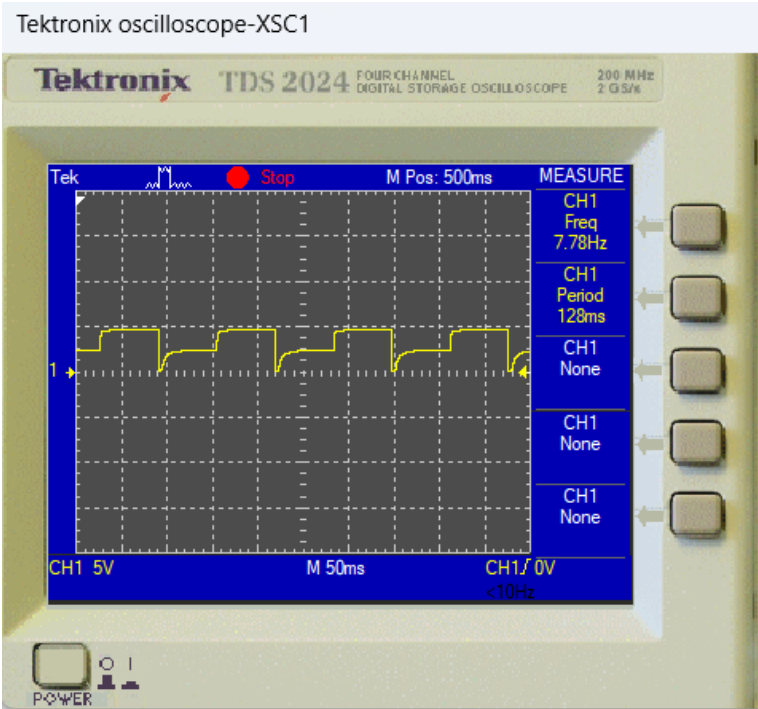


Figure 3-14: Circuit's output for 5 Hz

3.4.3 Breadboard Design

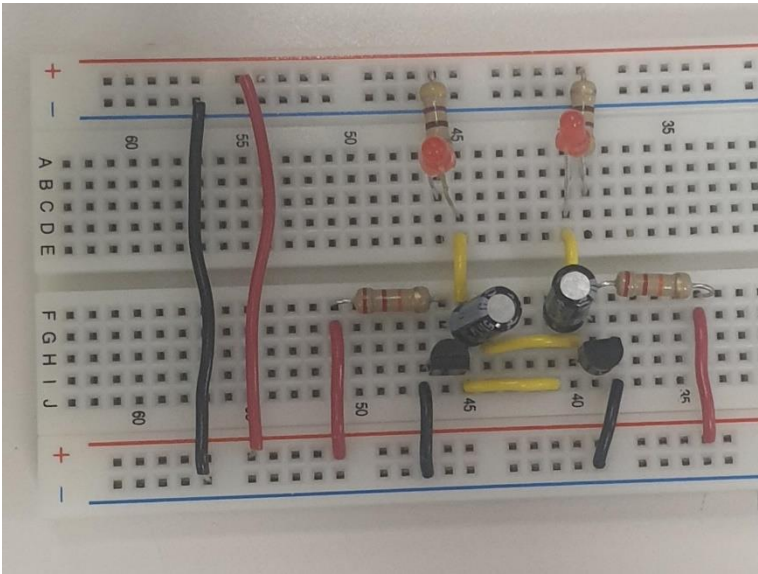


Figure 3-15: Breadboard's design for 5 Hz



3. Result

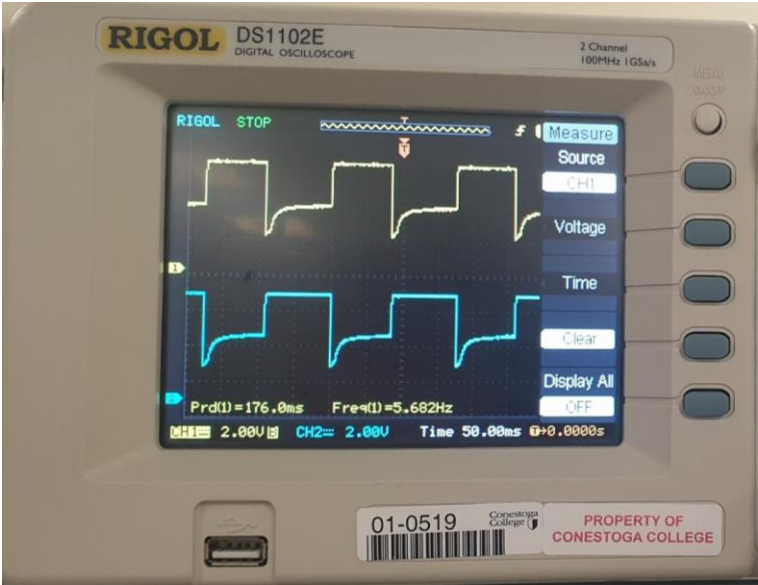


Figure 3-16: Breadboard's output for 5 Hz

3.4.4 Result

| Theory expected frequency (Hz) | Multisim expected frequency (Hz) | Breadboard expected frequency (Hz) |
|--------------------------------|----------------------------------|------------------------------------|
| 6.56 Hz                        | 7.78 Hz                          | 5.682 Hz                           |

Table 3-4: Result for 5 Hz

### 3. Result

#### 3.5 20 Hz (67% ON and 33% OFF)

##### 3.5.1 Calculation for equipment

To design an Astable Multivibrator with 25 Hz, the periodic time will be:

$$T = \frac{1}{f} = \frac{1}{20 \text{ Hz}} = 50 \text{ (ms)}$$

Let  $t_1$  is the duration of ON time and  $t_2$  is the duration of OFF time,

$$T = t_1 + t_2 = 3 \times t_2$$

$$t_2 = \frac{T}{3} = 16.67 \text{ (ms)}$$

$$t_1 = \frac{2 \times T}{3} = 33.33 \text{ (ms)}$$

From the result, choosing  $R_2 = 47\text{k}\Omega$ ,  $C_2 = 1\mu\text{F}$  and  $R_3 = 22\text{k}\Omega$ ,  $C_1 = 1\mu\text{F}$  will give the closest result:

$$t_1 = \ln(2) \times R_2 \times C_2 = 32.571 \text{ (ms)}$$

$$t_2 = \ln(2) \times R_3 \times C_1 = 15.247 \text{ (ms)}$$

$$f = \frac{1}{T} = \frac{1}{t_1 + t_2} = 20.91 \text{ (Hz)}$$

##### 3.5.2 Multisim Design

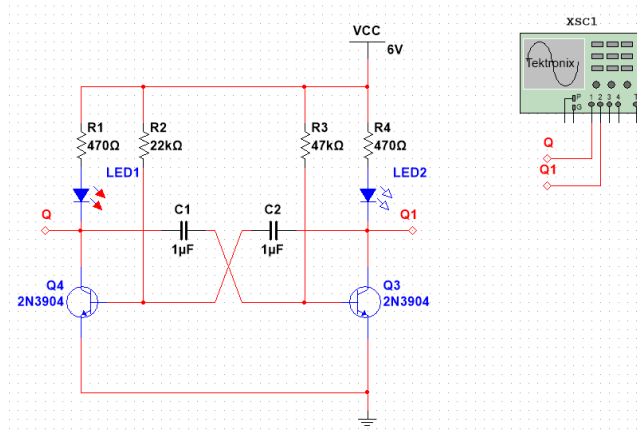


Figure 3-17: Circuit design with  $R_2 = 47\text{k}\Omega$ ,  $C_2 = 1\mu\text{F}$  and  $R_3 = 22\text{k}\Omega$ ,  $C_1 = 1\mu\text{F}$

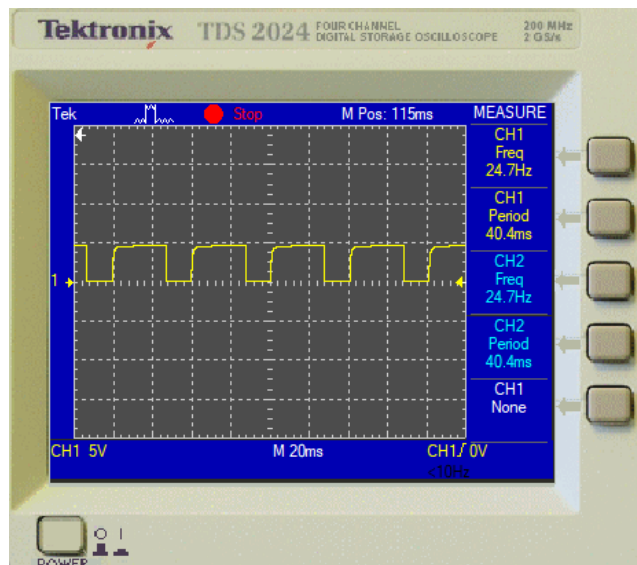


Figure 3-18: Circuit's output of Channel 1 for 20Hz (67% ON, 33% OFF time)

### 3. Result

Time: 20ms/div

From figure 3-14, T taken up 2 squares with  $t_1$  occupied 3/5 square and  $t_2$  occupied 7/5 square so,

$$t_1 = \frac{3 \times T}{10} = 12 \text{ (ms) (ON time)}$$

$$t_2 = \frac{7 \times T}{10} = 28 \text{ (ms) (OFF time)}$$

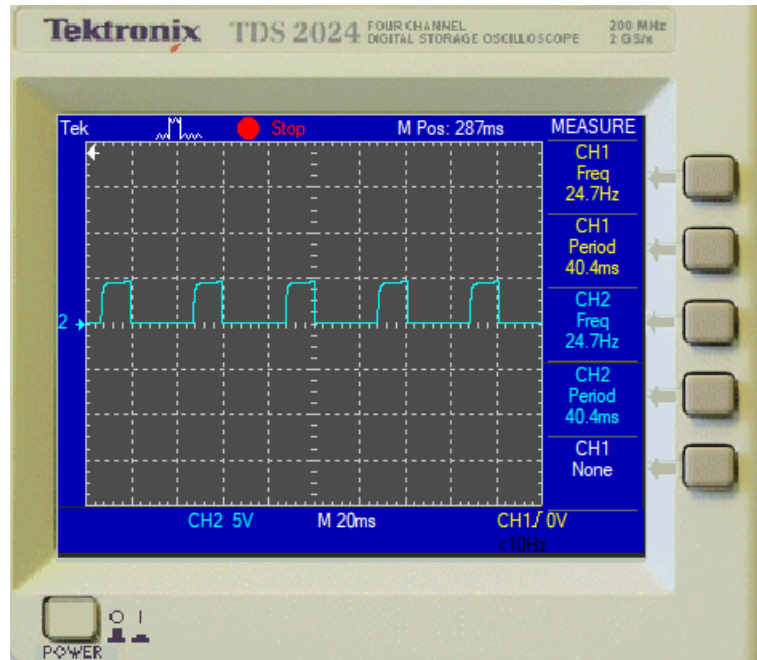


Figure 3-19: Circuit's output of Chanel 2 for 20Hz (33% ON, 67% OFF)

Time: 20ms/div

From figure 3-14, T taken up 2 squares with  $t_1$  occupied 3/5 square and  $t_2$  occupied 7/5 square so,

$$t_1 = \frac{7 \times T}{10} = 12 \text{ (ms) (ON time)}$$

$$t_2 = \frac{3 \times T}{10} = 28 \text{ (ms) (OFF time)}$$

### 3. Result

#### 3.5.3 Breadboard Design

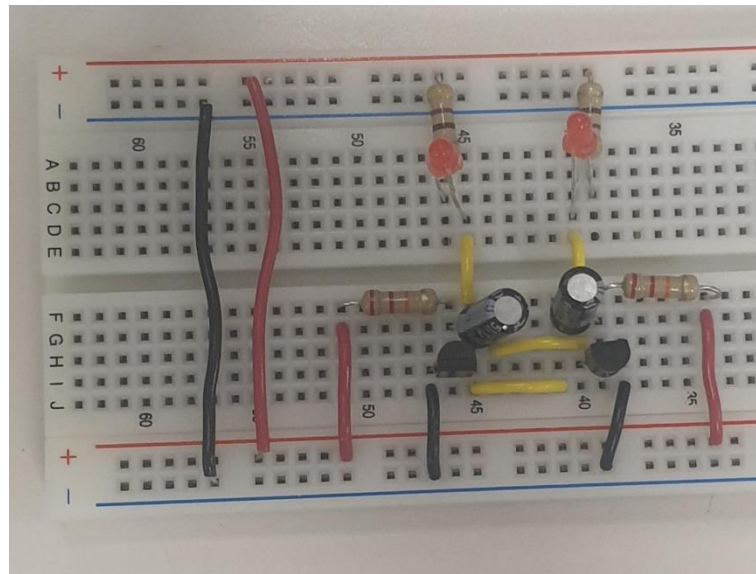


Figure 3-20: Breadboard's design for 20 Hz

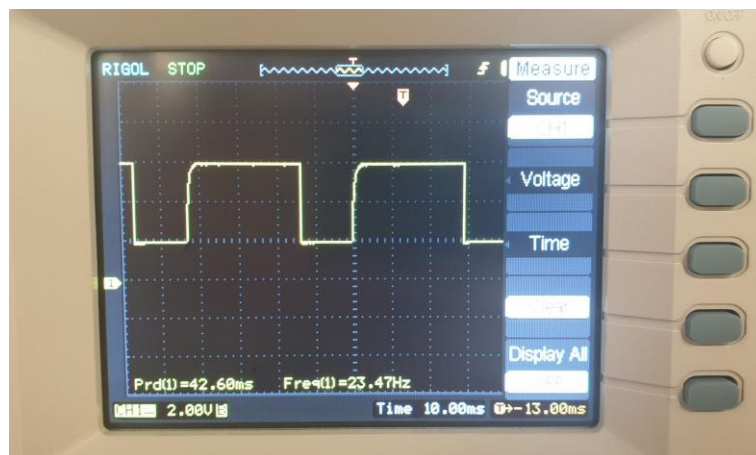


Figure 3-21: Breadboard's output for 20Hz (Channel 1)

Time: 10ms/div

From figure 3-14, T taken up 4.2 squares with  $t_1$  occupied 3 square and  $t_2$  occupied 1.2 square so,

$$t_1 = \frac{3 \times T}{4.2} = 30.43 \text{ (ms) (ON time)}$$

$$t_2 = \frac{1.2 \times T}{4.2} = 12.17 \text{ (ms) (OFF time)}$$

3. Result

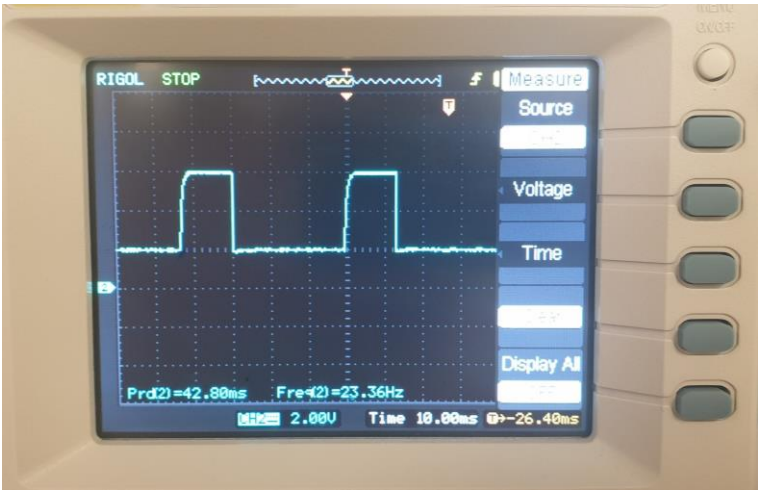


Figure 3-22: Breadboard's output for 20Hz (Channel 2)

Time: 10ms/div

From figure 3-14, T taken up 4.2 squares with  $t_1$  occupied 1.2 square and  $t_2$  occupied 3 square so,

$$t_1 = \frac{1.2 \times T}{4.2} = 12.17 \text{ (ms) (ON time)}$$
$$t_2 = \frac{3 \times T}{4.2} = 30.43 \text{ (ms) (OFF time)}$$

3.5.4 Result

| Theory expected frequency (Hz)                         | Multisim expected frequency (Hz) (Channel 1)  | Breadboard expected frequency (Hz) (Channel 1)       |
|--------------------------------------------------------|-----------------------------------------------|------------------------------------------------------|
| f = 20.91 Hz<br>$t_1$ = 32.571 ms<br>$t_2$ = 15.247 ms | f = 24.7 Hz<br>$t_1$ = 28 ms<br>$t_2$ = 12 ms | f = 23.47 Hz<br>$t_1$ = 30.43 ms<br>$t_2$ = 12.17 ms |

Table 3-5: Result for 20 Hz

### 4. CONCLUSION

From the result of all 5 cases:

- All 5 cases have Multisim's result and Breadboard's result nearly the same.
- Although there is a slight big difference when comparing the error of Theory's with Multisim's and Multisim's with Breadboard's, the error is still acceptable.

REFERENCES