

LAB NOTE

Subject: Digital Design Principles

Topic: Magnitude Comparator

Student: Minh Quan Tran

July 12th, 2024

Table of Contents

1. Objectives.....	4
2. Theory and Design.....	6
2.1 Theory	6
2.2 Requirement	6
2.3 Solution	6
3. VHDL and Verilog	6
3.1 VHDL code	6
3.2 Verilog code	9
4. Pin Planner.....	14
4.1 Input and Output.....	14
5. Result	16

TABLE OF FIGURES

Figure 2-1: Octal Decoder's Truth Table.....	6
Figure 4-1: SCEMA5F31C6N board	14
Figure 4-2: SW0 and SW1 Pin No	15
Figure 4-3: LEDR0's Pin No	15
Figure 4-4: HEX's Pin No	15
Figure 5-1: When input = '000'.	16
Figure 5-2: When input = '111'	16
Figure 5-3: When input '101'	17
Figure 5-4: Input '101' with Complement mode	17
Figure 5-5: Input '101' with Multiline mode	18
Figure 5-6: Result for adding them up	18

1. Objectives

1. Objectives

- Design a Magnitude Comparator using Quartus software.
- Write a VHDL and Verilog code from the design.
- Push the code and run to the SCEMA5F31C6N board.

2. Theory and Design

2. Theory and Design

2.1 Theory

Magnitude Comparator is a circuit that compare 2 inputs A and B and give out either 3 output '100', '010' and '001' which should represent Greater Than, Equal, Less Than.

2.2 Requirement

- Use VHDL and Verilog to implement a Magnitude Comparator and display to LED [0:2].
- Introduction to the VHDL Case statement.
- **Above and beyond:** Adding mode: Clock count up from 00:00:00 to 23:59:59 with 2 speed normal speed and 100x speed.

2.3 Solution

To design this system, first need to identify input and output:

- Input will be from SW0 to SW7.
- Output will be LED[2:0].

Then identify what the output will be, from the 2 inputs,

TRUTH TABLE									
COMPARING INPUTS				CASCADING INPUTS			OUTPUTS		
A ₃ B ₃	A ₂ B ₂	A ₁ B ₁	A ₀ B ₀	I _{A>B}	I _{A<B}	I _{A=B}	O _{A>B}	O _{A<B}	O _{A=B}
A ₃ >B ₃	X	X	X	X	X	X	H	L	L
A ₃ <B ₃	X	X	X	X	X	X	L	H	L
A ₃ =B ₃	A ₂ >B ₂	X	X	X	X	X	H	L	L
A ₃ =B ₃	A ₂ <B ₂	X	X	X	X	X	L	H	L
A ₃ =B ₃	A ₂ =B ₂	A ₁ >B ₁	X	X	X	X	H	L	L
A ₃ =B ₃	A ₂ =B ₂	A ₁ <B ₁	X	X	X	X	L	H	L
A ₃ =B ₃	A ₂ =B ₂	A ₁ =B ₁	A ₀ >B ₀	X	X	X	H	L	L
A ₃ =B ₃	A ₂ =B ₂	A ₁ =B ₁	A ₀ <B ₀	X	X	X	L	H	L
A ₃ =B ₃	A ₂ =B ₂	A ₁ =B ₁	A ₀ =B ₀	H	L	L	H	L	L
A ₃ =B ₃	A ₂ =B ₂	A ₁ =B ₁	A ₀ =B ₀	L	H	L	L	H	L
A ₃ =B ₃	A ₂ =B ₂	A ₁ =B ₁	A ₀ =B ₀	X	X	H	L	L	H
A ₃ =B ₃	A ₂ =B ₂	A ₁ =B ₁	A ₀ =B ₀	H	H	L	L	L	L
A ₃ =B ₃	A ₂ =B ₂	A ₁ =B ₁	A ₀ =B ₀	L	L	L	H	H	L

Figure 2-1: Magnitude Comparator's Truth Table

3. VHDL and Verilog

3.1 VHDL code

3.1.1 Top entity

```
library ieee;
use ieee.std_logic_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity MTran_Lab7_VHDL_MagnitudeComparator is
port
(
    -- Inputs
    CLOCK_50 : in std_logic;
    A         : in std_logic_vector (3 downto 0);
    B         : in std_logic_vector (3 downto 0);
    mode      : in std_logic;

    -- Outputs
    LED       : out std_logic_vector (2 downto 0);
    HEX0      : out std_logic_vector (6 downto 0);
    HEX1      : out std_logic_vector (6 downto 0);
    HEX2      : out std_logic_vector (6 downto 0);
    HEX3      : out std_logic_vector (6 downto 0);
    HEX4      : out std_logic_vector (6 downto 0);
    HEX5      : out std_logic_vector (6 downto 0)
);
end entity;

architecture Behavioral of MTran_Lab7_VHDL_MagnitudeComparator is

-- Module declaration
component MTran_Lab7_VHDL_Timer is
port
(
    -- Inputs
    Clk       : in std_logic;
    Enable    : in std_logic;

    -- Outputs
    Seconds   : inout integer;
    Minutes   : inout integer;
    Hours     : inout integer
);
end component;

-- Singal declaration
signal intA      : integer := 0;
signal intB      : integer := 0;

signal Enable    : std_logic;

signal Seconds   : integer := 0;
signal Minutes   : integer := 0;
signal Hours     : integer := 0;

-- Function
function SevenSegmentDisplay(Number : integer) return std_logic_vector is
```

3. VHDL and Verilog

```
begin
  case (Number) is
    when 0 => return "1000000";
    when 1 => return "1111001";
    when 2 => return "0100100";
    when 3 => return "0110000";
    when 4 => return "0011001";
    when 5 => return "0010010";
    when 6 => return "0000010";
    when 7 => return "1111000";
    when 8 => return "0000000";
    when 9 => return "0010000";
    when others => return "1111111";
  end case;
end SevenSegmentDisplay;

-- Main code
begin
  -- Module instantiate
  module_timer: MTran_Lab7_VHDL_Timer
  port map
  (
    Clk      => CLOCK_50,
    Enable   => Enable,
    Seconds  => Seconds,
    Minutes  => Minutes,
    Hours    => Hours
  );

  -- Process
  process (CLOCK_50, Seconds, Minutes, Hours, A, B) is
  begin
    if mode = '0' then
      -- Disable Timer
      Enable <= '0';

      -- Reset HEX2
      HEX2 <= "1111111";

      -- Convert A and B from std_logic to integer
      intA <= to_integer(unsigned(A));
      intB <= to_integer(unsigned(B));

      -- Display A and B in decimal

      -- A
      HEX0 <= SevenSegmentDisplay(intA mod 10);
      HEX1 <= SevenSegmentDisplay(intA / 10);

      -- B
      HEX4 <= SevenSegmentDisplay(intB mod 10);
      HEX5 <= SevenSegmentDisplay(intB / 10);

      -- Compare A and B
      if intA > intB then
        LED <= "100";
        HEX3 <= "0100111";
      elsif intA = intB then
        LED <= "010";
        HEX3 <= "0110111";
      else

```

3. VHDL and Verilog

```
        LED <= "001";
        HEX3 <= "0110011";
    end if;

    else
        Enable <= '1';
        LED <= "000";
        -- Display Second
        HEX0 <= SevenSegmentDisplay(Seconds mod 10);
        HEX1 <= SevenSegmentDisplay(Seconds / 10);

        -- Display Minute
        HEX2 <= SevenSegmentDisplay(Minutes mod 10);
        HEX3 <= SevenSegmentDisplay(Minutes / 10);

        -- Display Hour
        HEX4 <= SevenSegmentDisplay(Hours mod 10);
        HEX5 <= SevenSegmentDisplay(Hours / 10);

    end if;

end process;

end architecture;
```

3.1.2 Component Timer

```
library ieee;
use ieee.std_logic_1164.ALL;

entity MTran_Lab7_VHDL_Timer is
port
(
    -- Inputs
    Clk      : in    std_logic;
    Enable   : in    std_logic;

    -- Outputs
    Seconds  : inout integer := 0;
    Minutes  : inout integer := 0;
    Hours    : inout integer := 0
);
end entity;

architecture RTL of MTran_Lab7_VHDL_Timer is

    -- Signal Declaration
    signal Ticks                : integer := 0;

    -- Procedure
    procedure Increment( signal Counter    : inout integer;
                        constant MaxValue  : in    integer;
                        variable ResetFlag : out   boolean) is
    begin
        if Counter = MaxValue - 1 then
            -- Reset Counter
            Counter <= 0;
            ResetFlag := True;
        else
            Counter <= Counter + 1;
        end if;
    end procedure;

end architecture;
```


3. VHDL and Verilog

```
        ResetFlag := False;
    end if;
end procedure;

begin

    process(Clk, Enable) is

        -- Variable Declaring
        variable SecondsFlag      : boolean := false;
        variable MinutesFlag      : boolean := false;
        variable HoursFlag        : boolean := false;

        constant MaxSeconds       : integer := 60;
        constant MaxMinutes       : integer := 60;
        constant MaxHours         : integer := 24;

        constant ClockFrequency   : integer := 50000000;

        -- Main
    begin

        if Enable = '1' then
            if rising_edge(Clk) then

                -- Increment Ticks
                Increment(Ticks, ClockFrequency, SecondsFlag);

                -- Increment Seconds whenever Ticks reach Clock Frequency
                if SecondsFlag then
                    Increment(Seconds, MaxSeconds, MinutesFlag);
                end if;

                -- Increment Minute whenever 60 seconds
                if SecondsFlag and MinutesFlag then
                    Increment(Minutes, MaxMinutes, HoursFlag);
                end if;

                -- Increment Hours whenever 60 minutes
                if SecondsFlag and MinutesFlag and HoursFlag then
                    Increment(Hours, MaxHours, HoursFlag);
                end if;
            end if;
        end if;

    end process;
end architecture;
```

3.2 Verilog code

3.2.1 Top Module

```
module MTran_Lab7_Verilog_MagnitudeComparator
(
    input wire CLOCK_50,
    input wire [3:0] A,
    input wire [3:0] B,
    input mode,
    input speed,
    output reg [2:0] LED,
    output reg [6:0] HEX0,
    output reg [6:0] HEX1,

```

3. VHDL and Verilog

```
    output reg [6:0] HEX2,
    output reg [6:0] HEX3,
    output reg [6:0] HEX4,
    output reg [6:0] HEX5
);

// Signals declaration
reg [31:0] intA;
reg [31:0] intB;

reg Enable;

wire [31:0] Seconds1;
wire [31:0] Minutes1;
wire [31:0] Hours1;

wire [31:0] Seconds2;
wire [31:0] Minutes2;
wire [31:0] Hours2;

// Module Instantiation
MTran_Lab7_Verilog_Timer
#(
    .MAXSECONDS(60),
    .MAXMINUTES(60),
    .MAXHOURS(24),
    .CLKFREQUENCY(500000) // 500kHz => Clock 10 times faster
)

Tim1
(
    .Clk(CLOCK_50),
    .Enable(Enable),
    .Seconds(Seconds1),
    .Minutes(Minutes1),
    .Hours(Hours1)
);

MTran_Lab7_Verilog_Timer
#(
    .MAXSECONDS(60),
    .MAXMINUTES(60),
    .MAXHOURS(24),
    .CLKFREQUENCY(50000000) // 50 MHz => Normal Clk
)

Tim2
(
    .Clk(CLOCK_50),
    .Enable(Enable),
    .Seconds(Seconds2),
    .Minutes(Minutes2),
    .Hours(Hours2)
);

// Function for Seven Segment Display
function [6:0] SevenSegmentDisplay;
    input [3:0] Number;
    begin
        case (Number)
            4'h0: SevenSegmentDisplay = 7'b1000000;
            4'h1: SevenSegmentDisplay = 7'b1111001;
            4'h2: SevenSegmentDisplay = 7'b0100100;
```

3. VHDL and Verilog

```
        4'h3: SevenSegmentDisplay = 7'b0110000;
        4'h4: SevenSegmentDisplay = 7'b0011001;
        4'h5: SevenSegmentDisplay = 7'b0010010;
        4'h6: SevenSegmentDisplay = 7'b0000010;
        4'h7: SevenSegmentDisplay = 7'b1111000;
        4'h8: SevenSegmentDisplay = 7'b0000000;
        4'h9: SevenSegmentDisplay = 7'b0010000;
        default: SevenSegmentDisplay = 7'b1111111;
    endcase
end
endfunction

always @(posedge CLOCK_50)
begin
    if (mode == 1'b0)
        begin
            // Disable Timer
            Enable = 1'b0;

            // Reset HEX2
            HEX2 = 7'b1111111;

            // Convert A and B from std_logic to integer
            intA = A;
            intB = B;

            // Display A and B in decimal
            // A
            HEX0 = SevenSegmentDisplay(intA % 10);
            HEX1 = SevenSegmentDisplay(intA / 10);

            // B
            HEX4 = SevenSegmentDisplay(intB % 10);
            HEX5 = SevenSegmentDisplay(intB / 10);

            // Compare A and B
            if (intA > intB)
                begin
                    LED = 3'b100;
                    HEX3 = 7'b0100111;
                end
            else if (intA == intB)
                begin
                    LED = 3'b010;
                    HEX3 = 7'b0110111;
                end
            else
                begin
                    LED = 3'b001;
                    HEX3 = 7'b0110011;
                end
            end
        end
    else
        begin
            Enable = 1'b1;
            LED = 3'b000;

            if (speed == 1'b0) //normal mode
                begin
```

3. VHDL and Verilog

```
// Display Second
HEX0  = SevenSegmentDisplay(Seconds2 % 10);
HEX1  = SevenSegmentDisplay(Seconds2 / 10);

// Display Minute
HEX2  = SevenSegmentDisplay(Minutes2 % 10);
HEX3  = SevenSegmentDisplay(Minutes2 / 10);

// Display Hour
HEX4  = SevenSegmentDisplay(Hours2 % 10);
HEX5  = SevenSegmentDisplay(Hours2 / 10);
end
else if (speed == 1'b1)
begin
    // Display Second
    HEX0  = SevenSegmentDisplay(Seconds1 % 10);
    HEX1  = SevenSegmentDisplay(Seconds1 / 10);

    // Display Minute
    HEX2  = SevenSegmentDisplay(Minutes1 % 10);
    HEX3  = SevenSegmentDisplay(Minutes1 / 10);

    // Display Hour
    HEX4  = SevenSegmentDisplay(Hours1 % 10);
    HEX5  = SevenSegmentDisplay(Hours1 / 10);
end
end
end
endmodule
```

3.2.2 Module Timer

```
module MTran_Lab7_Verilog_Timer

#(
    parameter MAXSECONDS      = 60,
    parameter MAXMINUTES     = 60,
    parameter MAXHOURS       = 24,
    parameter CLKFREQUENCY    = 50000000
)

(
    input wire Clk,
    input wire Enable,
    inout reg [31:0] Seconds,
    inout reg [31:0] Minutes,
    inout reg [31:0] Hours
);

// Signal Declaration
reg [31:0] Ticks = 0;

// Main Logic
always @(posedge Clk)
begin
    if (Enable)
    begin
        // Increment Ticks
        Ticks = Ticks + 1;
        if (Ticks == CLKFREQUENCY - 1)
        begin
```

3. VHDL and Verilog

```
        Ticks    = 0;
        Seconds  = Seconds + 1;
    end

    if (Seconds == MAXSECONDS)
        begin
            Seconds = 0;
            Minutes = Minutes + 1;
        end

    if (Minutes == MAXMINUTES)
        begin
            Minutes = 0;
            Hours   = Hours + 1;
        end

    if (Hours == MAXHOURS)
        begin
            Hours   = 0;
        end
    end
end
endmodule
```

4. Pin Planner

4.1 Input and Output

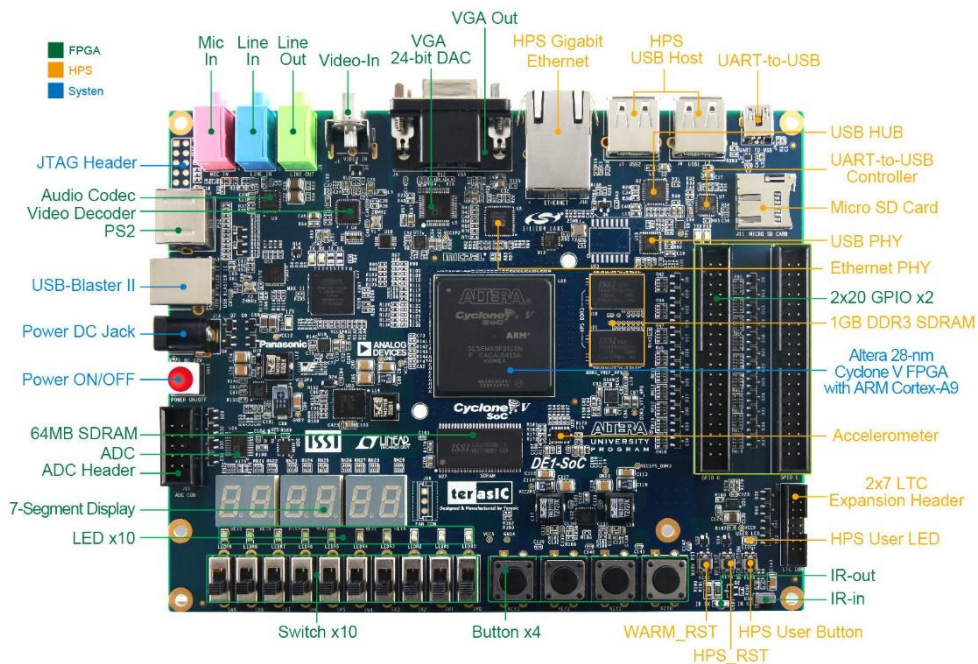


Figure 4-1: SCEMA5F31C6N board

Assigning:

SW[0]: SW0
SW[1]: SW1
SW[2]: SW2

Mode[0]: SW7
Mode[1]: SW8
EN: SW9

LED[0]: LEDR0
LED[1]: LEDR1
LED[2]: LEDR2
LED[3]: LEDR3
LED[4]: LEDR4
LED[5]: LEDR5
LED[6]: LEDR6
LED[7]: LEDR7

HEX0[0]: HEX0[0]
HEX0[1]: HEX0[1]
HEX0[2]: HEX0[2]
HEX0[3]: HEX0[3]
HEX0[4]: HEX0[4]
HEX0[5]: HEX0[5]
HEX0[6]: HEX0[6]

4. Pin Planner

From the DE1_SoC_User_Manual,

<i>Signal Name</i>	<i>FPGA Pin No.</i>	<i>Description</i>	<i>I/O Standard</i>
SW[0]	PIN_AB12	Slide Switch[0]	3.3V
SW[1]	PIN_AC12	Slide Switch[1]	3.3V
SW[2]	PIN_AF9	Slide Switch[2]	3.3V
SW[3]	PIN_AF10	Slide Switch[3]	3.3V
SW[4]	PIN_AD11	Slide Switch[4]	3.3V
SW[5]	PIN_AD12	Slide Switch[5]	3.3V

Figure 4-2: SW0 and SW1 Pin No

<i>Signal Name</i>	<i>FPGA Pin No.</i>	<i>Description</i>	<i>I/O Standard</i>
LEDR[0]	PIN_V16	LED [0]	3.3V
LEDR[1]	PIN_W16	LED [1]	3.3V

Figure 4-3: LEDR0's Pin No

<i>Signal Name</i>	<i>FPGA Pin No.</i>	<i>Description</i>	<i>I/O Standard</i>
HEX0[0]	PIN_AE26	Seven Segment Digit 0[0]	3.3V
HEX0[1]	PIN_AE27	Seven Segment Digit 0[1]	3.3V
HEX0[2]	PIN_AE28	Seven Segment Digit 0[2]	3.3V
HEX0[3]	PIN_AG27	Seven Segment Digit 0[3]	3.3V
HEX0[4]	PIN_AF28	Seven Segment Digit 0[4]	3.3V
HEX0[5]	PIN_AG28	Seven Segment Digit 0[5]	3.3V
HEX0[6]	PIN_AH28	Seven Segment Digit 0[6]	3.3V

Figure 4-4: HEX's Pin No

5. Result

 


Figure 5-1: When input = '000'.

$SW2 = 0$, $SW1 = 0$, $SW0 = 0$ which should be 0, **LED0** asserted and the 7 segment LED displaying **0**.

 


Figure 5-2: When input = '111'

$SW2 = 1$, $SW1 = 1$, $SW0 = 1$ which should be 7, **LED7** asserted and the 7 segment LED displaying **7**.

5. Result

 


Figure 5-3: When input '101'

SW2 = 1, SW1 = 0, SW0 = 1 which should be 5, **LED5** asserted and the 7 segment LED displaying 5.

Different mode:

- Complement mode:

 


Figure 5-4: Input '101' with Complement mode

In this mode, rather than LED5 assert, all other LED except LED5 asserted. To activate this mode SW [8:7] = '01'.

5. Result

- Multiline Mode:

 


Figure 5-5: Input '101' with Multiline mode

In this mode, when input is '101' which is 5, LED0 to LED5 lit up. To activate this mode SW [8:7] = '10'.

- Complement Multiline Mode:

 


Figure 5-6: Result for adding them up

In this mode, it take the output of Multiline Mode and complemented it. To activate this mode SW [8:7] = '11'

REFERENCES