

# LAB NOTE

**Subject: Digital Design Principles**

**Topic: Shift Register**

**Student: Minh Quan Tran**

**July 26<sup>th</sup>, 2024**

# Table of Contents

<b>1. Objectives .....</b>	<b>4</b>
<b>2. Theory and Design.....</b>	<b>6</b>
2.1 Theory .....	6
2.2 Requirement .....	6
2.3 Solution .....	6
<b>3. VHDL and Verilog .....</b>	<b>6</b>
3.1 VHDL code .....	6
3.1.1 Top entity .....	6
3.2 Verilog code .....	8
<b>4. Pin Planner.....</b>	<b>10</b>
4.1 Input and Output.....	10
<b>5. Result .....</b>	<b>12</b>

## TABLE OF FIGURES

Figure 2-1: Shift Register's Truth Table .....	6
Figure 4-1: SCEMA5F31C6N board .....	10
Figure 4-2: SW0 and SW1 Pin No .....	11
Figure 4-3: LEDR0's Pin No .....	11
Figure 4-4: HEX's Pin No .....	11
Figure 5-1: When input = '000' .....	12
Figure 5-2: When input = '111' .....	12
Figure 5-3: When input '101' .....	13
Figure 5-4: Input '101' with Complement mode .....	13
Figure 5-5: Input '101' with Multiline mode .....	14
Figure 5-6: Result for adding them up .....	14

## **1. Objectives**

---

### **1. Objectives**

- Design a Counters using Quartus software.
- Write a VHDL and Verilog code from the design.
- Push the code and run to the SCEMA5F31C6N board.

## 2. Theory and Design

## 2. Theory and Design

### 2.1 Theory

A shift register is a digital circuit used for storing and transferring data, consisting of a series of flip-flops connected in a chain. Data is shifted through these flip-flops sequentially, either left or right, with each clock pulse. There are various types of shift registers, including Serial-In Serial-Out (SISO), Serial-In Parallel-Out (SIPO), Parallel-In Serial-Out (PISO), and Parallel-In Parallel-Out (PIPO), each serving different data input and output requirements. Shift registers are crucial in digital systems for tasks such as data storage, data transfer, and data conversion between serial and parallel formats.

### 2.2 Requirement

- Use VHDL and Verilog to implement the shift and display to LED [1:4].
- Introduction to the VHDL Case statement.
- **Above and beyond:** Adding Complement mode

### 2.3 Solution

To design this system, first need to identify input and output:

- Input will be from BTN0 to BTN3
  - o BTN0 : CLK
  - o BTN1 : Speed
  - o BTN3 : Reset

- Output will be LED[4:1].

Then identify what the output will be, from the 2 inputs,

MODE SELECT — TRUTH TABLE										
OPERATING MODE	INPUTS						OUTPUTS			
	MR	S <sub>1</sub>	S <sub>0</sub>	D <sub>SR</sub>	D <sub>SL</sub>	P <sub>n</sub>	Q <sub>0</sub>	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>
Reset	L	X	X	X	X	X	L	L	L	L
Hold	H	l	l	X	X	X	q <sub>0</sub>	q <sub>1</sub>	q <sub>2</sub>	q <sub>3</sub>
Shift Left	H	h	l	X	l	X	q <sub>1</sub>	q <sub>2</sub>	q <sub>3</sub>	L
	H	h	l	X	h	X	q <sub>1</sub>	q <sub>2</sub>	q <sub>3</sub>	H
Shift Right	H	l	h	l	X	X	L	q <sub>0</sub>	q <sub>1</sub>	q <sub>2</sub>
	H	l	h	h	X	X	H	q <sub>0</sub>	q <sub>1</sub>	q <sub>2</sub>
Parallel Load	H	h	h	X	X	P <sub>0</sub>	P <sub>0</sub>	P <sub>1</sub>	P <sub>2</sub>	P <sub>3</sub>

L = LOW Voltage Level  
H = HIGH Voltage Level  
X = Don't Care  
l = LOW voltage level one set-up time prior to the LOW to HIGH clock transition  
h = HIGH voltage level one set-up time prior to the LOW to HIGH clock transition  
P<sub>n</sub> (q<sub>n</sub>) = Lower case letters indicate the state of the referenced input (or output) one set-up time prior to the LOW to HIGH clock transition.

Figure 2-1: Shift Register's Truth Table

## 3. VHDL and Verilog

### 3.1 VHDL code

#### 3.1.1 Top entity

```
library ieee;
use ieee.std_logic_1164.all;

entity MTran_Lab9_VHDL_ShiftRegister is
port
(
    -- Inputs
    BTN    : in std_logic;
    Speed  : in std_logic;
    Reset  : in std_logic;
    SW     : in std_logic_vector (7 downto 0);

    -- Outputs
    LED    : out std_logic_vector (3 downto 0);
    HEX0   : out std_logic_vector (6 downto 0)
);
end entity;

architecture behavioral of MTran_Lab9_VHDL_ShiftRegister is

    -- Signal Declaration
    signal Counter : integer           := 1;

    signal Output  : std_logic_vector (3 downto 0) := "0000";
    signal Sel     : std_logic_vector (1 downto 0);

    -- Function declaration
    function SevenSegmentDisplay (Number : integer) return std_logic_vector is
    begin
        case (Number) is
            when 0    => return "1000000";
            when 1    => return "1111001";
            when 2    => return "0100100";
            when 3    => return "0110000";
            when 4    => return "0011001";
            when 5    => return "0010010";
            when 6    => return "0000010";
            when 7    => return "1111000";
            when 8    => return "0000000";
            when 9    => return "0010000";
            when others => return "1111111";
        end case;
    end SevenSegmentDisplay;

begin

    -- Process

    -- Check Sel
    process (SW(6), SW(7)) is
    begin
        Sel <= SW(7) & SW(6);
    end process;
```

### 3. VHDL and Verilog

---

```
-- Check Speed
process(Speed) is
begin
    if Speed ='0' then
        if Counter < 4 then
            Counter <= Counter * 2;
        else
            Counter <= 1;
        end if;
    end if;

end process;

-- Main code (Shift)
process(Sel, SW, BTN, Reset) is
begin

-- Reset BTN
if Reset = '0' then
    Output <= "0000";
elsif rising_edge(BTN) then
    if Counter = 1 then

        case (Sel) is
        when "00" => NULL;
        when "01" => Output <= Output(2 downto 0) & SW(0);
        when "10" => Output <= SW(5) & Output(3 downto 1);
        when "11" => Output <= SW(4 downto 1);
        end case;
    elsif Counter = 2 then

        case (Sel) is
        when "00" => NULL;
        when "01" => Output <= Output(1 downto 0) & SW(0) & SW(0);
        when "10" => Output <= SW(5) & SW(5) & Output(3 downto 2);
        when "11" => Output <= SW(4 downto 1);
        end case;

    elsif Counter = 4 then
        case (Sel) is
        when "00" => NULL;
        when "01" => Output <= SW(0) & SW(0) & SW(0) & SW(0);
        when "10" => Output <= SW(5) & SW(5) & SW(5) & SW(5);
        when "11" => Output <= SW(4 downto 1);
        end case;

    end if;
end if;
end process;

-- Output
process(Output, Counter)
begin
    LED <= Output;
    HEX0 <= SevenSegmentDisplay(Counter);
end process;
end Behavioral;
```

### 3. VHDL and Verilog

---

#### 3.2 Verilog code

```
module MTran_Lab9_Verilog_ShiftRegister
(
    input wire BTN,
    input wire Speed,
    input wire Reset,
    input wire [7:0] SW,
    output reg [3:0] LED,
    output reg [6:0] HEX0
);

    // Signal Declarations
    reg [3:0] Output;
    reg [1:0] Sel;
    integer Counter = 1;

    // Seven Segment Display function
    function [6:0] SevenSegmentDisplay;
        input integer Number;
        begin
            case (Number)
                0: SevenSegmentDisplay = 7'b1000000;
                1: SevenSegmentDisplay = 7'b1111001;
                2: SevenSegmentDisplay = 7'b0100100;
                3: SevenSegmentDisplay = 7'b0110000;
                4: SevenSegmentDisplay = 7'b0011001;
                5: SevenSegmentDisplay = 7'b0010010;
                6: SevenSegmentDisplay = 7'b0000010;
                7: SevenSegmentDisplay = 7'b1111000;
                8: SevenSegmentDisplay = 7'b0000000;
                9: SevenSegmentDisplay = 7'b0010000;
                default: SevenSegmentDisplay = 7'b1111111;
            endcase
        end
    endfunction

    // Check Sel
    always @(*)
        begin
            Sel = {SW[7], SW[6]};
        end

    // Check Speed
    always @(negedge Speed)
        begin
            if (Speed == 0)
                begin
                    if (Counter < 4)
                        Counter = Counter * 2;
                    else
                        Counter = 1;
                end
            end
        end

    // Main code (Shift)
    always @(negedge BTN or negedge Reset)
        begin
            if (Reset == 0)
                Output <= 4'b0000;
            else if (BTN == 0)
                begin
```



### 3. VHDL and Verilog

---

```
        if (Counter == 1)
            begin
                case (Sel)
                    2'b00: Output = Output;
                    2'b01: Output = {Output[2:0], SW[0]};
                    2'b10: Output = {SW[5], Output[3:1]};
                    2'b11: Output = SW[4:1];
                endcase
            end
            else if (Counter == 2)
                begin
                    case (Sel)
                        2'b00: Output = Output;
                        2'b01: Output = {Output[1:0], SW[0], SW[0]};
                        2'b10: Output = {SW[5], SW[5], Output[3:2]};
                        2'b11: Output = SW[4:1];
                    endcase
                end
            else if (Counter == 4)
                begin
                    case (Sel)
                        2'b00: Output = Output;
                        2'b01: Output = {SW[0], SW[0], SW[0], SW[0]};
                        2'b10: Output = {SW[5], SW[5], SW[5], SW[5]};
                        2'b11: Output = SW[4:1];
                    endcase
                end
            end
        end
    end

// Output
always @(*)
    begin
        LED = Output;
        HEX0 = SevenSegmentDisplay(Counter);
    end
endmodule
```

### 4. Pin Planner

#### 4.1 Input and Output

 


Figure 4-1: SCEMA5F31C6N board

Assigning:

SW[0]: SW0  
SW[1]: SW1  
SW[2]: SW2

Mode[0]: SW7  
Mode[1]: SW8  
EN: SW9

LED[0]: LEDR0  
LED[1]: LEDR1  
LED[2]: LEDR2  
LED[3]: LEDR3  
LED[4]: LEDR4  
LED[5]: LEDR5  
LED[6]: LEDR6  
LED[7]: LEDR7

HEX0[0]: HEX0[0]  
HEX0[1]: HEX0[1]  
HEX0[2]: HEX0[2]  
HEX0[3]: HEX0[3]  
HEX0[4]: HEX0[4]  
HEX0[5]: HEX0[5]  
HEX0[6]: HEX0[6]

## 4. Pin Planner

From the DE1\_SoC\_User\_Manual,

<i>Signal Name</i>	<i>FPGA Pin No.</i>	<i>Description</i>	<i>I/O Standard</i>
SW[0]	PIN_AB12	Slide Switch[0]	3.3V
SW[1]	PIN_AC12	Slide Switch[1]	3.3V
SW[2]	PIN_AF9	Slide Switch[2]	3.3V
SW[3]	PIN_AF10	Slide Switch[3]	3.3V
SW[4]	PIN_AD11	Slide Switch[4]	3.3V
SW[5]	PIN_AD12	Slide Switch[5]	3.3V

Figure 4-2: SW0 and SW1 Pin No

<i>Signal Name</i>	<i>FPGA Pin No.</i>	<i>Description</i>	<i>I/O Standard</i>
LEDR[0]	PIN_V16	LED [0]	3.3V
LEDR[1]	PIN_W16	LED [1]	3.3V

Figure 4-3: LEDR0's Pin No

<i>Signal Name</i>	<i>FPGA Pin No.</i>	<i>Description</i>	<i>I/O Standard</i>
HEX0[0]	PIN_AE26	Seven Segment Digit 0[0]	3.3V
HEX0[1]	PIN_AE27	Seven Segment Digit 0[1]	3.3V
HEX0[2]	PIN_AE28	Seven Segment Digit 0[2]	3.3V
HEX0[3]	PIN_AG27	Seven Segment Digit 0[3]	3.3V
HEX0[4]	PIN_AF28	Seven Segment Digit 0[4]	3.3V
HEX0[5]	PIN_AG28	Seven Segment Digit 0[5]	3.3V
HEX0[6]	PIN_AH28	Seven Segment Digit 0[6]	3.3V

Figure 4-4: HEX's Pin No

## 5. Result

 


Figure 5-1: When input = '000'.

$SW2 = 0$ ,  $SW1 = 0$ ,  $SW0 = 0$  which should be 0, **LED0** asserted and the 7 segment LED displaying **0**.

 


Figure 5-2: When input = '111'

$SW2 = 1$ ,  $SW1 = 1$ ,  $SW0 = 1$  which should be 7, **LED7** asserted and the 7 segment LED displaying **7**.



## 5. Result

 


Figure 5-3: When input '101'

SW2 = 1, SW1 = 0, SW0 = 1 which should be 5, **LED5** asserted and the 7 segment LED displaying 5.

Different mode:

- Complement mode:

 


Figure 5-4: Input '101' with Complement mode

In this mode, rather than LED5 assert, all other LED except LED5 asserted. To activate this mode SW [8:7] = '01'.

## 5. Result

### - Multiline Mode:

 


Figure 5-5: Input '101' with Multiline mode

In this mode, when input is '101' which is 5, LED0 to LED5 lit up. To activate this mode SW [8:7] = '10'.

### - Complement Multiline Mode:

 


Figure 5-6: Result for adding them up

In this mode, it take the output of Multiline Mode and complemented it. To activate this mode SW [8:7] = '11'

REFERENCES