

LAB NOTE

Subject: Digital Design Principles

Topic: Octal Decoder

Student: Minh Quan Tran

Jun 6th, 2024

Table of Contents

1. Objectives.....	4
2. Theory and Design.....	6
2.1 Theory	6
2.2 Requirement	6
2.3 Solution	6
3. VHDL and Verilog	6
3.1 VHDL code	6
3.2 Verilog code	7
4. Pin Planner.....	10
4.1 Input and Output.....	10
5. Result	12

TABLE OF FIGURES

Figure 2-1: Octal Decoder's Truth Table.....	6
Figure 4-1: SCEMA5F31C6N board	10
Figure 4-2: SW0 and SW1 Pin No	11
Figure 4-3: LEDR0's Pin No	11
Figure 4-4: HEX's Pin No	11
Figure 5-1: When input = '000'	12
Figure 5-2: When input = '111'	12
Figure 5-3: When input '101'	13
Figure 5-4: Input '101' with Complement mode	13
Figure 5-5: Input '101' with Multiline mode	14
Figure 5-6: Result for adding them up	14

1. Objectives

1. Objectives

- Design an Octal Decoder using Quartus software.
- Write a VHDL and Verilog code from the design.
- Push the code and run to the SCEMA5F31C6N board.

2. Theory and Design

2.1 Theory

Decoder circuit is a combinational logic circuit used to decode binary input. As an example consider the octal decoder depicted in fig.(1). It has three inputs; x2, x1, x0 and eight outputs y0 to y7. . Only one of the output lines is asserted at any time. The valuation of the binary number of the input lines: (x2, x1, x0) determines which output line is activated. Other names of the octal decoder are 3-to-8 decoder and 1-out-of-8 decoder. The truth table in fig. (2) demonstrates the relation between the outputs and the inputs of the decoder.

In any decoder, the index of the asserted output is always equal to the valuation of the binary number of the input lines. Applying 100 at the input lines (x2, x1, x0) will assert output y4 and leave all other outputs are de-asserted.

Number of input lines N of the decoder is calculated based on the number of outputs M:

$$N = \log_2 M$$

Other decoder circuits are the 2-to-4 decoder, decimal decoder, hexadecimal decoder.

2.2 Requirement

- Use VHDL and Verilog to implement an Octal Decoder and display to LED [0:7].
- Introduction to the VHDL Case statement.
- **Above and beyond:** Adding 3 more modes: Complement Mode, Multiline Mode, Complement Multiline Mode.

2.3 Solution

To design this system, first need to identify input and output:

- Input will be from SW0 to SW2.
- Output will be the 7 LED.

Then identify what the output will be from the 3 Switches,

Truth table of the octal decoder										
input			output							
x2	x1	x0	y7	y6	y5	y4	y3	y2	y1	y0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

Figure 2-1: Octal Decoder's Truth Table

3. VHDL and Verilog

3.1 VHDL code

```
library ieee;
use ieee.std_logic_1164.all;

-- Declaring input and output
entity MTran_Lab5_VHDL_OctalDecoder is
    port
    (
        EN      : in  std_logic;
        SW      : in  std_logic_vector (2 downto 0);
        mode    : in  std_logic_vector (1 downto 0);
        LED     : out std_logic_vector (7 downto 0);
        HEX     : out std_logic_vector (6 downto 0)
    );
end MTran_Lab5_VHDL_OctalDecoder;

-- Describing the relationship between output and input
architecture behavioral of MTran_Lab5_VHDL_OctalDecoder is

    -- Variable Declaring
    signal LED_output : std_logic_vector (7 downto 0) := "00000000";

    -- Function's Declaration

    -- Function for Octal Decoder
    function Decoder3to8_NormalMode(Switch: in std_logic_vector (2 downto 0)) return
    std_logic_vector is
    begin
        case Switch is
            when "000" => return "00000001";
            when "001" => return "00000010";
            when "010" => return "00000100";
            when "011" => return "00001000";
            when "100" => return "00010000";
            when "101" => return "00100000";
            when "110" => return "01000000";
            when "111" => return "10000000";
        end case;
    end Decoder3to8_NormalMode;

    function Decoder3to8_MultilineMode(Switch: in std_logic_vector (2 downto 0)) return
    std_logic_vector is
    begin
        case Switch is
            when "000" => return "00000001";
            when "001" => return "00000011";
            when "010" => return "00000111";
            when "011" => return "00001111";
            when "100" => return "00011111";
            when "101" => return "00111111";
            when "110" => return "01111111";
            when "111" => return "11111111";
        end case;
    end Decoder3to8_MultilineMode;

    -- Seven Segment Display
    function SevenSegmentDisplay(Switch : std_logic_vector (2 downto 0)) return
    std_logic_vector is
```

3. VHDL and Verilog

```
begin
  case Switch is
    when "000" => return "10000000";
    when "001" => return "1111001";
    when "010" => return "0100100";
    when "011" => return "0110000";
    when "100" => return "0011001";
    when "101" => return "0010010";
    when "110" => return "0000010";
    when "111" => return "1111000";
  end case;
end SevenSegmentDisplay;

begin
  process (SW, mode)
  begin
    if EN = '1' then
      case mode is

        -- Normal Mode
        when "00" =>
          LED <= Decoder3to8_NormalMode(SW);
          HEX <= SevenSegmentDisplay(SW);

        -- Complement Mode
        when "01" =>
          LED_output <= Decoder3to8_NormalMode(SW);
          HEX <= SevenSegmentDisplay(SW);
          LED <= not LED_output;

        -- Multiline Mode
        when "10" =>
          LED <= Decoder3to8_MultilineMode(SW);
          HEX <= SevenSegmentDisplay(SW);

        -- Complement Multiline Mode
        when "11" =>
          LED_output <= Decoder3to8_MultilineMode(SW);
          HEX <= SevenSegmentDisplay(SW);
          LED <= not LED_output;

      end case;
    else
      LED <= "00000000";
      HEX <= "1111111";
    end if;
  end process;
end behavioral;
```

3.2 Verilog code

```
module MTran_Lab5_Verilog_OctalDecoder (
  input EN,
  input [2:0] SW,
  input [1:0] mode,
  output reg [7:0] LED,
  output reg [6:0] HEX
);
```

3. VHDL and Verilog

```
// Variable Declaring
reg [7:0] LED_output;

// Function's Declaration

// Function for Octal Decoder
function [7:0] Decoder3to8_NormalMode;
input [2:0] Switch;
begin
    case (Switch)
        3'd0: Decoder3to8_NormalMode = 8'b00000001;
        3'd1: Decoder3to8_NormalMode = 8'b00000010;
        3'd2: Decoder3to8_NormalMode = 8'b00000100;
        3'd3: Decoder3to8_NormalMode = 8'b00001000;
        3'd4: Decoder3to8_NormalMode = 8'b00010000;
        3'd5: Decoder3to8_NormalMode = 8'b00100000;
        3'd6: Decoder3to8_NormalMode = 8'b01000000;
        3'd7: Decoder3to8_NormalMode = 8'b10000000;
        default: Decoder3to8_NormalMode = 8'b00000000;
    endcase
end
endfunction

function [7:0] Decoder3to8_MultilineMode;
input [2:0] Switch;
begin
    case (Switch)
        3'd0: Decoder3to8_MultilineMode = 8'b00000001;
        3'd1: Decoder3to8_MultilineMode = 8'b00000011;
        3'd2: Decoder3to8_MultilineMode = 8'b00000111;
        3'd3: Decoder3to8_MultilineMode = 8'b00001111;
        3'd4: Decoder3to8_MultilineMode = 8'b00011111;
        3'd5: Decoder3to8_MultilineMode = 8'b00111111;
        3'd6: Decoder3to8_MultilineMode = 8'b01111111;
        3'd7: Decoder3to8_MultilineMode = 8'b11111111;
        default: Decoder3to8_MultilineMode = 8'b00000000;
    endcase
end
endfunction

// Seven Segment Display
function [6:0] SevenSegmentDisplay;
input [2:0] Switch;
begin
    case (Switch)
        3'd0: SevenSegmentDisplay = 7'b1000000;
        3'd1: SevenSegmentDisplay = 7'b1111001;
        3'd2: SevenSegmentDisplay = 7'b0100100;
        3'd3: SevenSegmentDisplay = 7'b0110000;
        3'd4: SevenSegmentDisplay = 7'b0011001;
        3'd5: SevenSegmentDisplay = 7'b0010010;
        3'd6: SevenSegmentDisplay = 7'b0000010;
        3'd7: SevenSegmentDisplay = 7'b1111000;
        default: SevenSegmentDisplay = 7'b1111111;
    endcase
end
endfunction

// Main code
always @ (SW,EN,mode)
begin
    if (EN)
```


3. VHDL and Verilog

```
begin
    case (mode)

        // Normal Mode
        2'b00:
            begin
                LED = Decoder3to8_NormalMode(SW);
                HEX = SevenSegmentDisplay(SW);
            end

        // Complement Mode
        2'b01:
            begin
                LED_output = Decoder3to8_NormalMode(SW);
                HEX = SevenSegmentDisplay(SW);
                LED = ~LED_output;
            end

        // Multiline Mode
        2'b10:
            begin
                LED = Decoder3to8_MultilineMode(SW);
                HEX = SevenSegmentDisplay(SW);
            end

        // Complement Multiline Mode
        2'b11:
            begin
                LED_output = Decoder3to8_MultilineMode(SW);
                HEX = SevenSegmentDisplay(SW);
                LED = ~LED_output;
            end

    endcase
end
else
begin
    LED = 8'b00000000;
    HEX = 7'b1111111;
end
end
endmodule
```

4. Pin Planner

4.1 Input and Output

 


Figure 4-1: SCEMA5F31C6N board

Assigning:

SW[0]: SW0
SW[1]: SW1
SW[2]: SW2

Mode[0]: SW7
Mode[1]: SW8
EN: SW9

LED[0]: LEDR0
LED[1]: LEDR1
LED[2]: LEDR2
LED[3]: LEDR3
LED[4]: LEDR4
LED[5]: LEDR5
LED[6]: LEDR6
LED[7]: LEDR7

HEX0[0]: HEX0[0]
HEX0[1]: HEX0[1]
HEX0[2]: HEX0[2]
HEX0[3]: HEX0[3]
HEX0[4]: HEX0[4]
HEX0[5]: HEX0[5]
HEX0[6]: HEX0[6]

4. Pin Planner

From the DE1_SoC_User_Manual,

<i>Signal Name</i>	<i>FPGA Pin No.</i>	<i>Description</i>	<i>I/O Standard</i>
SW[0]	PIN_AB12	Slide Switch[0]	3.3V
SW[1]	PIN_AC12	Slide Switch[1]	3.3V
SW[2]	PIN_AF9	Slide Switch[2]	3.3V
SW[3]	PIN_AF10	Slide Switch[3]	3.3V
SW[4]	PIN_AD11	Slide Switch[4]	3.3V
SW[5]	PIN_AD12	Slide Switch[5]	3.3V

Figure 4-2: SW0 and SW1 Pin No

<i>Signal Name</i>	<i>FPGA Pin No.</i>	<i>Description</i>	<i>I/O Standard</i>
LEDR[0]	PIN_V16	LED [0]	3.3V
LEDR[1]	PIN_W16	LED [1]	3.3V

Figure 4-3: LEDR0's Pin No

<i>Signal Name</i>	<i>FPGA Pin No.</i>	<i>Description</i>	<i>I/O Standard</i>
HEX0[0]	PIN_AE26	Seven Segment Digit 0[0]	3.3V
HEX0[1]	PIN_AE27	Seven Segment Digit 0[1]	3.3V
HEX0[2]	PIN_AE28	Seven Segment Digit 0[2]	3.3V
HEX0[3]	PIN_AG27	Seven Segment Digit 0[3]	3.3V
HEX0[4]	PIN_AF28	Seven Segment Digit 0[4]	3.3V
HEX0[5]	PIN_AG28	Seven Segment Digit 0[5]	3.3V
HEX0[6]	PIN_AH28	Seven Segment Digit 0[6]	3.3V

Figure 4-4: HEX's Pin No

5. Result

 


Figure 5-1: When input = '000'.

$SW2 = 0$, $SW1 = 0$, $SW0 = 0$ which should be 0, **LED0** asserted and the 7 segment LED displaying **0**.

 


Figure 5-2: When input = '111'

$SW2 = 1$, $SW1 = 1$, $SW0 = 1$ which should be 7, **LED7** asserted and the 7 segment LED displaying **7**.

5. Result

 


Figure 5-3: When input '101'

SW2 = 1, SW1 = 0, SW0 = 1 which should be 5, **LED5** asserted and the 7 segment LED displaying 5.

Different mode:

- Complement mode:

 


Figure 5-4: Input '101' with Complement mode

In this mode, rather than LED5 assert, all other LED except LED5 asserted. To activate this mode SW [8:7] = '01'.

5. Result

- Multiline Mode:

 


Figure 5-5: Input '101' with Multiline mode

In this mode, when input is '101' which is 5, LED0 to LED5 lit up. To activate this mode SW [8:7] = '10'.

- Complement Multiline Mode:

 


Figure 5-6: Result for adding them up

In this mode, it take the output of Multiline Mode and complemented it. To activate this mode SW [8:7] = '11'

REFERENCES